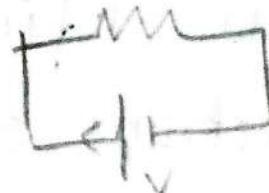


# UNIT-I Electric Circuit

Voltage: Potential difference b/w 2 points. (or) work done for moving a <sup>unit</sup> charge from one point to other point.

$$V = \frac{W}{q}$$



It is defined as the potential difference b/w any two points known as voltage.

voltage is denoted by 'V' and the unit of voltage is volts.

(or)

voltage is defined as work done in moving unit charge from one point to other point.

$$V = \frac{W}{q} = \frac{\text{Joules}}{\text{coulomb}} \Rightarrow \text{Volts.}$$

Units of voltage is Volts & voltage is denoted by V.

$$V = \frac{dW}{dq}$$

current: Rate of flow of charge or  
Rate of flow of electrons.

(i) or 'I' is the denotion.

Unit : Ampere

It is defined as rate of flow  
of electrons or charge known as  
current and current is represented  
by 'I' or (i) and the unit  
of current is amperes.

$$\boxed{I = \frac{q}{t} = \frac{\text{coulombs}}{\text{sec}} = \text{Amp.}}$$
$$= \frac{dq}{dt}$$

Energy (W): Capacity to do the  
work.

Energy is nothing but capacity  
to do work it is represented by  
'W' & unit of energy is joules.

$$W = \int P \cdot dt$$

$$W = \int P \cdot dt$$

Power: Power is nothing but energy with respect to time (or) product of voltage and current.  $P = \frac{V \cdot I}{A}$

Power is denoted by 'P'.  
units of power is watts.

$$\boxed{\text{Power} = \frac{\text{Work done}}{\text{Time}} = \frac{\text{Energy}}{\text{Time}} = \frac{W}{t}}$$

$$\text{Power} = \frac{\text{Energy}}{\text{time}} = \text{watts}$$

$$P = V \times I$$

$$P = \frac{dW}{dQ} \times \frac{dQ}{dt}$$

$$\boxed{P = \frac{dW}{dt}}$$

$$W = P \times t$$

Ohm's law: It states that at constant temperature current is directly proportional to voltage and inversely

proportional to resistance known as Ohm's law

current is directly  $\propto V$

$$I \propto V$$

$$I \propto \frac{1}{R}$$

$$V = IR \propto V$$

$$I \propto V$$

$$I \propto \frac{1}{R}$$

$$I = \frac{V}{R} A$$

$$V = IR A$$

$$R = \frac{V}{I} \Omega$$

$$I = \frac{V}{R} V$$

$$R = \frac{V}{I} \Omega$$

Power formulae:  $P = V \times R$   $P = V \times I$   $P = I \times R$   
 $P = V \times I = IR \times I$

Energy:

$$W = \int P dt = \int V \times I dt$$

$$W = \int I^2 R dt$$

$$W = I^2 R t$$

$$\begin{aligned} W &= \int P dt \\ &= \int V \times I dt \\ &= I^2 R t \end{aligned}$$

$$V = I^2 R$$

$$= V \times \frac{V}{R}$$

$$P = \frac{V^2}{R}$$

watts

Limitations: Nature of the material

- 1) Ohm's law is not applicable to non linear circuits like SCR, diodes, transistors, Ohm's law also depends on the nature of the material.
- 2) Ohm's law is also not applicable to metals.

Temperature also effects Ohm's law.

Problems:

- 1) A 12 Ω resistor is connected across 6 volts battery find how much current flows through the resistor.

$$V = I R.$$

$$6 = I \times 12$$

$$I = \frac{6}{12}$$

$$I = 0.5 \text{ Amp.}$$

- 2) If 0.6 A current flows through a resistor voltage of 2 points of a resistor is 12 volts. What's the resistance of resistor.  $I = 0.6 \text{ A}$

$$R = \frac{V}{I} = \frac{12}{0.6} = 20 \Omega$$

30) If charge of a material is 30 coulombs  
we take the time 5 sec.  $I = ?$

$$I = \frac{Q}{t} = \frac{30}{5} = 6 \text{ Amp}$$

Resistor: Resistor is nothing but  
resistor opposes the very flow  
of current through it

It is denoted by  $R$ .

units = ohm ( $\Omega$ )

$$R = \frac{\rho l}{A}$$

$\rho$  = specific resistance (or)  
factors effecting resistors: resistivity.

1) Resistance depends upon length of  
the material

$$R \propto l$$

2) Area of Gross section

Resistance depends upon area of

Cross section  $R = \frac{1}{\sigma}$

$$R = \frac{\rho l}{a}$$

$\rho$  : specific resistance or resistivity.

$l$  : length

$a$  : cross sectional area.

Conductance ( $G$ ): It is the reciprocal of resistance. Denoted by  $g$ .

$$G = \frac{1}{R}$$

$$= \frac{1}{\Omega}$$

$$= \Omega^{-1} \text{ (or) Mho. (v)}$$

Unit of conductance is mho

Resistivity: It is defined as resistance of unit area and unit length it is denoted by ' $\rho$ ' & the units are 'ohm-m' ( $\Omega\text{-m}$ )

$$R = \frac{\rho l}{A}$$

$$\boxed{\rho = \frac{Ra}{l}} \text{ resistance per unit area by unit length}$$

$$\rho = \frac{\text{ohm-m}^2}{\text{m}} = \text{ohm-m.}$$

conductivity!

It is defined as reciprocal of resistivity,  
it is represented by ' $\sigma$ '. Unit of  
conductivity is  $\boxed{\sigma = \frac{1}{\rho}}$ .

Determine the resistance of 564 m  
length of aluminium conductor  
whose rectangular cross section is  
4 cm x 2 cm assume resistivity is  
equal to  $2.826 \times 10^{-8}$  ohm-m

$$2.826 \times 10^{-8} = R \times \frac{8 \times 10^{-4}}{53.16 - 7.232}$$

$$\frac{2.826 \times 10^{-8} \times 564}{23.8 \times 10^{-4}} = R.$$

$$= 1.413 \times 141 \times 10^{-4}$$

1413

$$R = 1.99233 \times 10^{-8} \Omega$$

141

Q) calculate the length of copper wire 1.5mm in diameter to have a resistance of 0.3 ohm

$$\frac{1413}{1413} \times 10^{-8} \times \frac{\pi d^2}{4} \times l = 0.3$$

the resistivity of  $\mu\text{m}\cdot\text{m}$ . 1.99233  
copper is 0.017 mohm

$$R = \frac{l}{A} = \frac{1.5 \times 10^{-3}}{\frac{\pi d^2}{4}} \times l = \frac{\pi d^2 l}{4}$$

$$R = 0.3 \Omega$$

$$\frac{\pi d^2 l}{4} = 0.017 \times 10^{-6}$$

$$A = \frac{\pi d^2}{4}$$

$$= \frac{3.14 \times 1.5 \times 1.5 \times 10^{-6}}{4}$$

2)

$$\frac{2 \times 3.14 (1.5)^2}{10} = 1.57 \times 0.75 \times 1.5 \times 10^{-6}$$

$$= 1.76625 \times 10^{-6}$$

$$R = \frac{SL}{A}$$

$$U = 10^{-6} \text{ m}, Q = 0.017 \times 10^{-6} \times 1$$


1 meter = 100 cm  
1 cm = 10 mm

$$= \frac{0.017 \times 10^{-6} \times 100}{1.76625 \times 10^{-6}}$$

$$I = \frac{0.3 \times 1.76625 \times 10^{-6}}{0.017 \times 10^{-6}}$$

$$I = 31.19 \text{ A}$$

Inductor (L): It does not allow any sudden change of current through it. It stores energy in the form of electromagnetic field. It is denoted by 'L'. It is a storage element. When a wire is wound forms L. Unit of Inductor is Henry (H).

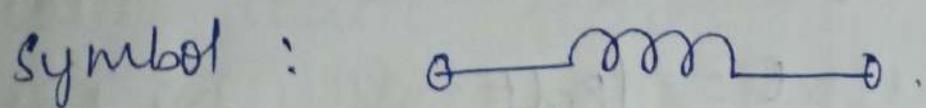Symbol : 

$V \propto I$  (from Ohm's law)  
voltage across inductor

$$V \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

L  
Henry (A)

$$V = L \frac{di}{dt}$$

current across the inductor:

$$\frac{di}{dt} = \frac{V}{L}$$

$$\frac{V}{L} = \frac{di}{dt}$$

$$\int di = \int \frac{V}{L} dt$$

$$\int di = \int \frac{V}{L} dt$$

$$i = \frac{1}{L} \int V dt$$

$$i = \frac{1}{L} [Vt]$$

Power across the inductor

$$P = V \times I$$

$$= L \frac{di}{dt} \times I$$

$$P = VI$$

$$= L \frac{di}{dt} V$$

$$\boxed{P = IL \frac{di}{dt}}$$

Energy stored in inductor

$$E = \int P dt$$

$$= \int IL \frac{di}{dt} dt$$

$$= L \int I di$$

$$\star \boxed{E = \frac{L I^2}{2}}$$

When the inductor is connected to the battery it stores its energy in the form of electromagnetic field & when the battery is removed it provides its energy to the circuit or to the capacitor.


## Capacitor (C) :

It is a passive circuit element.  
It works on the principle of capacitance.

Capacitor is a storage element which stores energy in the form of electro static field.

It is denoted by 'c'

Unit of capacitor is Faraday (F)

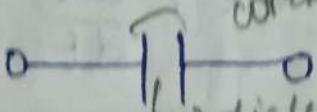Symbol:  made by conducting material  
UF  
mF

Current stored in the capacitor:

Note: It stores energy in the form of electrostatic field

It does not allow the sudden change of voltage in the circuit.

$$V = \frac{q}{C} \quad q = C V \quad i = C \frac{dV}{dt}$$

$$\frac{dV}{dt} = \frac{1}{C} \frac{dq}{dt} \quad i = \frac{dq}{dt} = \frac{d}{dt}(CV) \quad i = C \frac{dV}{dt}$$

$$i = C \frac{dv}{dt}$$

voltage across the capacitor:

$$\frac{dv}{dt} = \frac{1}{C} i$$

$$\int dv = \int i dt$$

$$v = \frac{1}{C} \int i dt$$

voltage across the capacitor:

$$P = V \times I$$

$$= V \times C \frac{dv}{dt}$$

$$P = C v \frac{dv}{dt}$$

Energy across the capacitor:

$$E = \int P dt$$

$$= \int C v \frac{dv}{dt} dt$$

$$E = \frac{1}{2} C v^2$$

## Types of Elements:

- capable to deliver energy
- (i) Active & Passive
  - not capable to provide energy but store energy
  - (ii) linear & non linear
  - (iii) lumped & distributed.
  - (iv) Unilateral & Bilateral.

Active & Passive elements: for a very long time


Active elements: capable to provide energy  
There are nothing but energy sources like voltage and current

source & the passive elements include Resistor, Inductor, capacitor. They are not capable of providing energy for a very long period of time

Linear & Non linear  
I & V characteristics of these types of elements which passes through the origin and satisfies superposition


theorem, principle & ohm's law.  
Principle known as linear elements:

Ex: R, L, C.

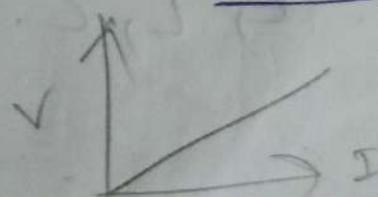

Non linear:  
In current & voltage characteristics of these types of elements does not pass through origin & Does not satisfy superposition theorem, Principle called Non linear elements.

Ex: Semiconductors like diodes.

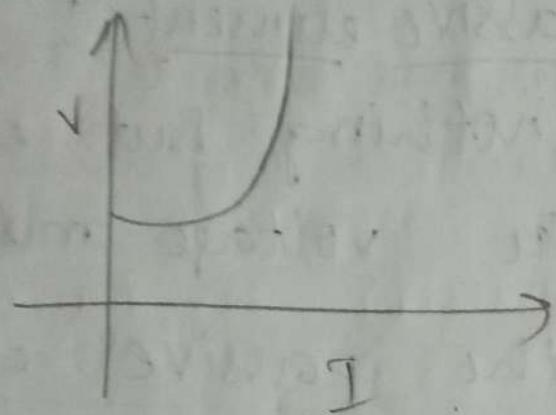

(iii) Lumped & distributed elements)

↓ ↓ parameters  
physically separable non physically  
small size dev ill. separable.

Lumped elements: which are very small in size and we can separate it easily.

Ex: R, L, C.

Distributed elements:

size is very high which cannot be separated physically


Ex: Transmission lines.

(iv) unilateral & bilateral elements:

current passes from anode to cathode.

Elements which can conduct current in only one direction known as unilateral elements.

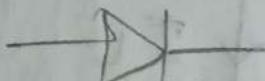Ex: Diode, SCR (Silicon control rectifier)



anode, cathode are terminals


Elements which are having two directions or which can conduct current in both the directions known as bilateral elements.

Ex: R, L, C.


Types of sources:

Independent

(i) Independent

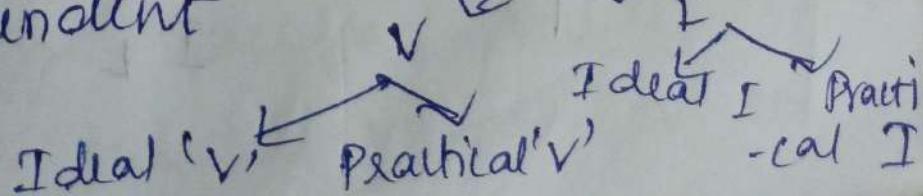

(ii) Dependent

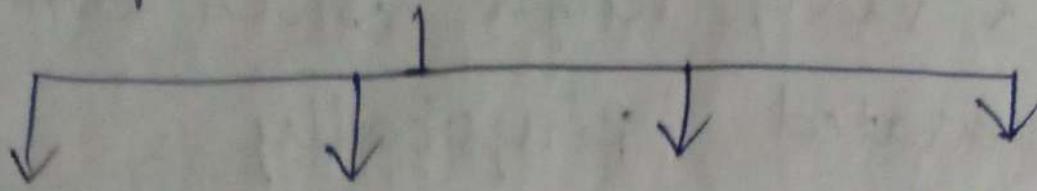

VDVS



VDCS



CDVS

CDVS.

voltage voltage current current  
dependent dependent dependent dependent  
voltage current current voltage  
source source source source.

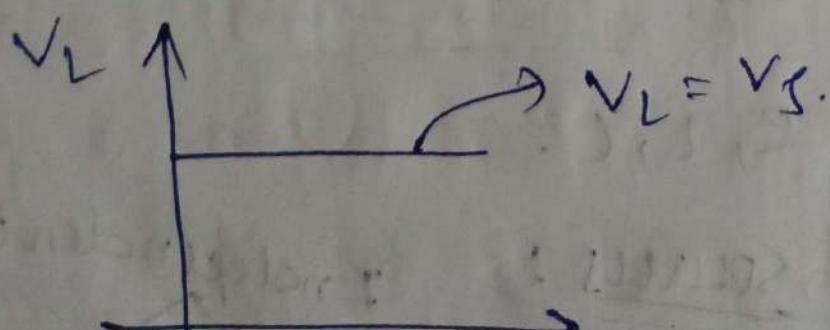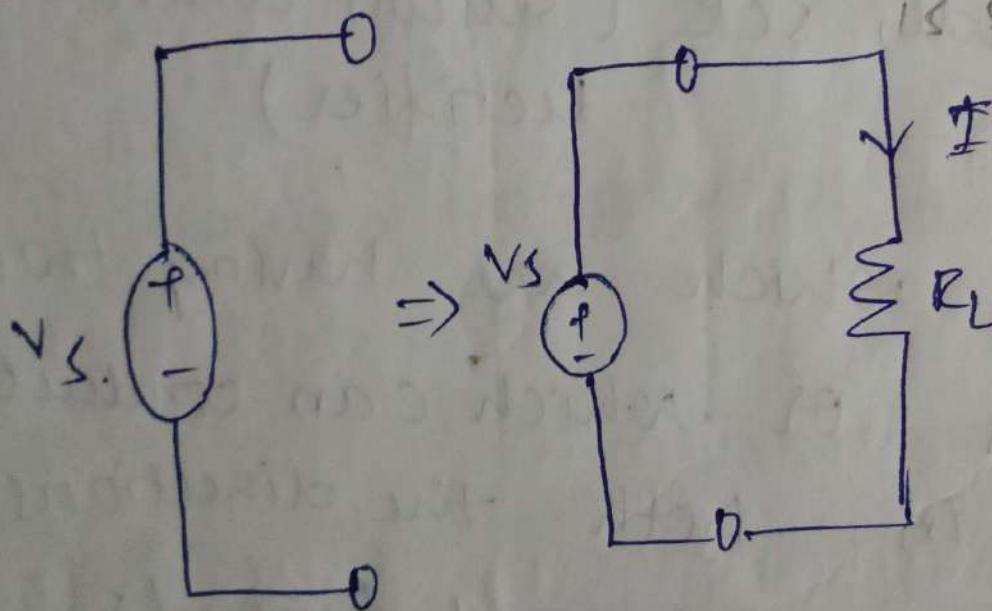① Ideal (V) source: Voltage across  
the load & source  
is same irrespective  
of difference  
in current



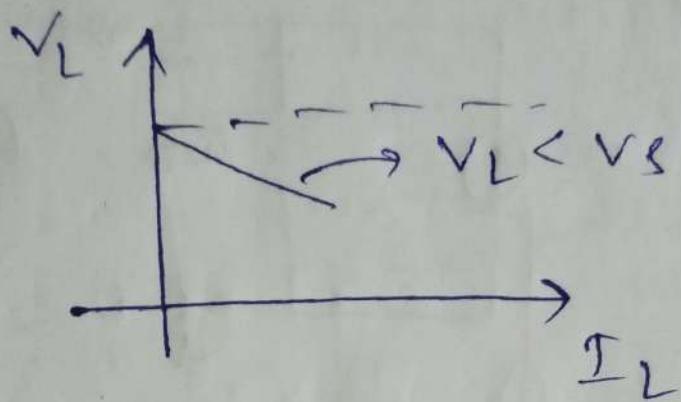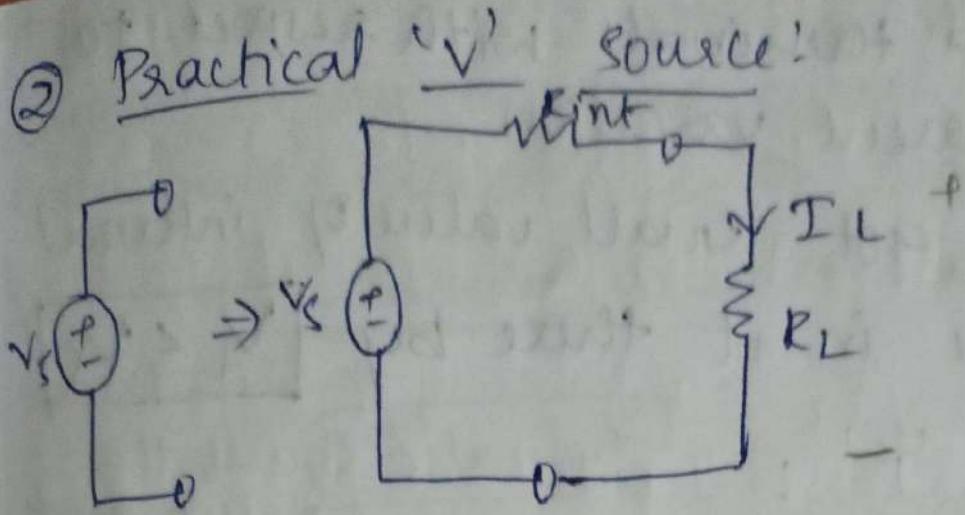

① Ideal voltage source:

It is a voltage source which gives constant voltage to the load terminals irrespective of load current variation

$$[V_L = V_s]$$





② Practical voltage source:

It is the voltage source which delivers the specified value of voltage or reduced voltage to the

the load terminals with respect to  
load current variation.

It has got small value of internal  
resistance in it hence by  $V_L < V_S$

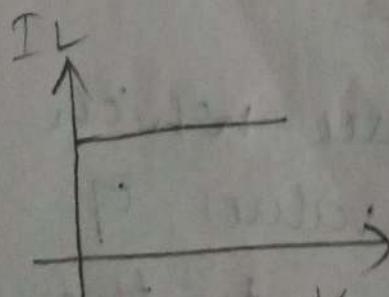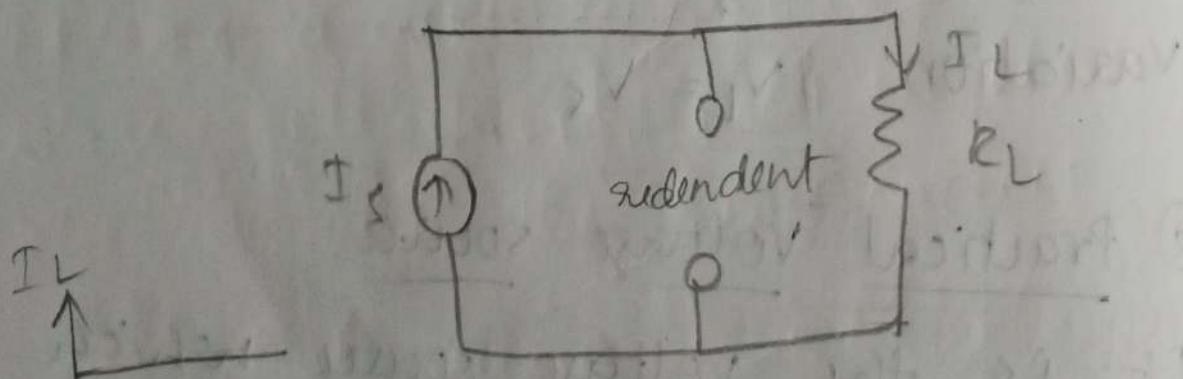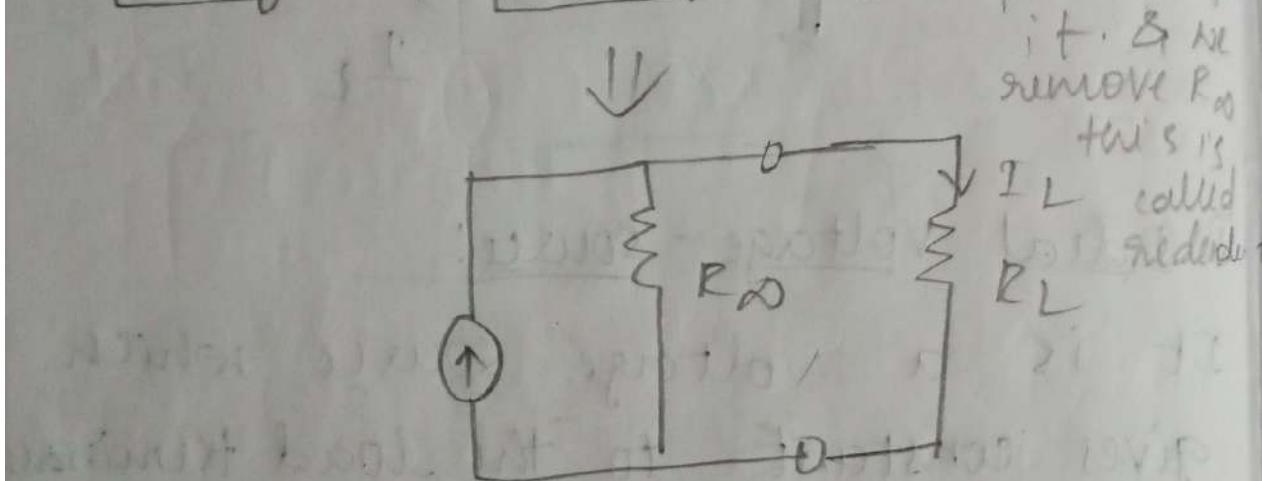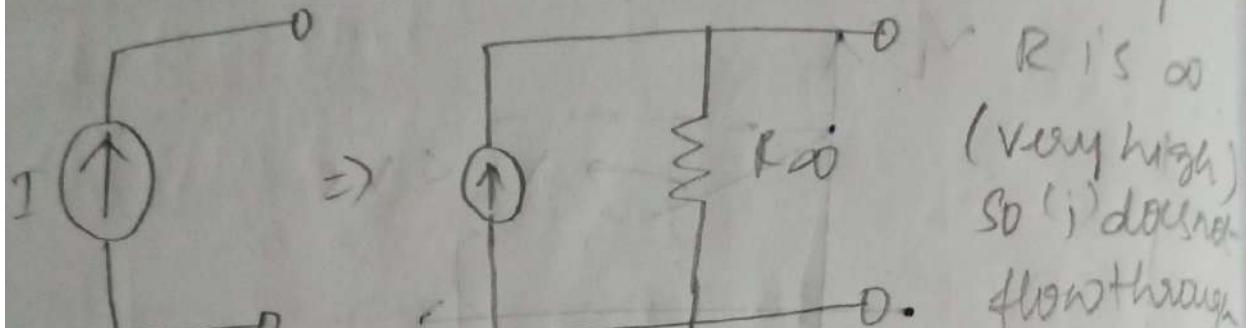
(iii) Ideal T: In ideal case the  
value of





It is a current source which delivers constant value of load current to load terminals irrespective of load variation. It has infinite value of internal resistance.

$$I_L = I_s$$

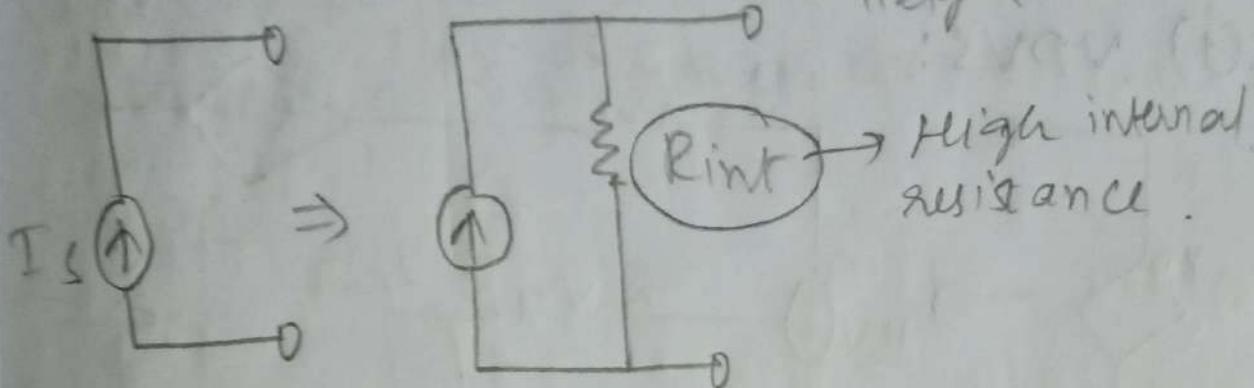(iv) Practical I: In current source int resistor is connected inely.



High internal resistance.

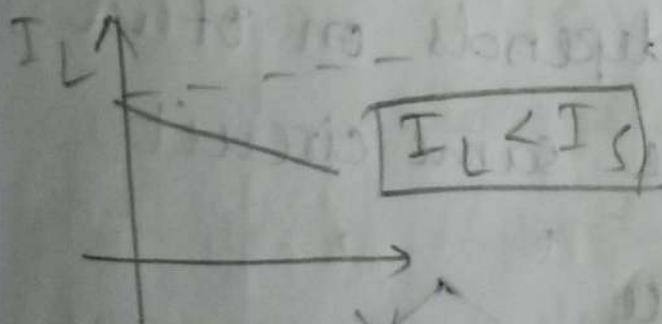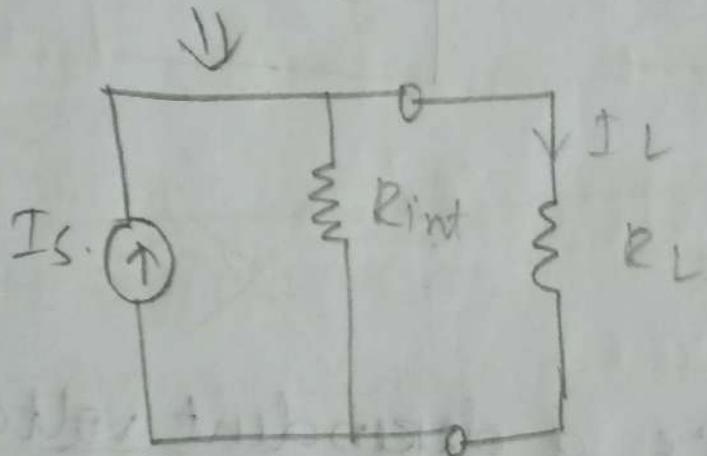


It is a current source which delivers specified value of current or

reduced value of current to load terminals w.r.t load voltage variation  
→ It has got high internal resistance



$$[I_L < I_S]$$

(i) Dependent:

(ii) VDVS:

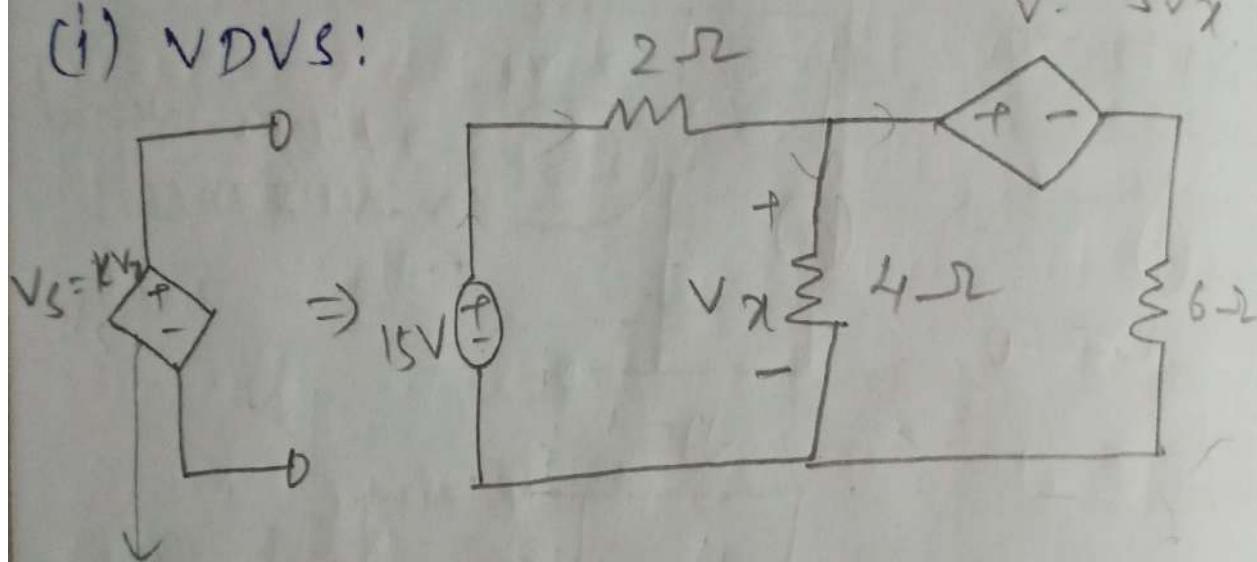


dependent voltage source

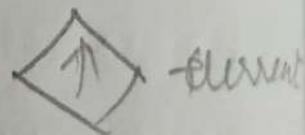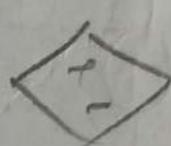


It is a dependent voltage source whose voltage depends on other element <sup>voltage</sup> in the same circuit

Dependent source

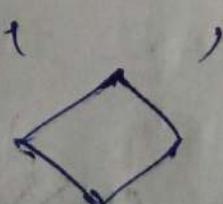


(ii) VDIS:

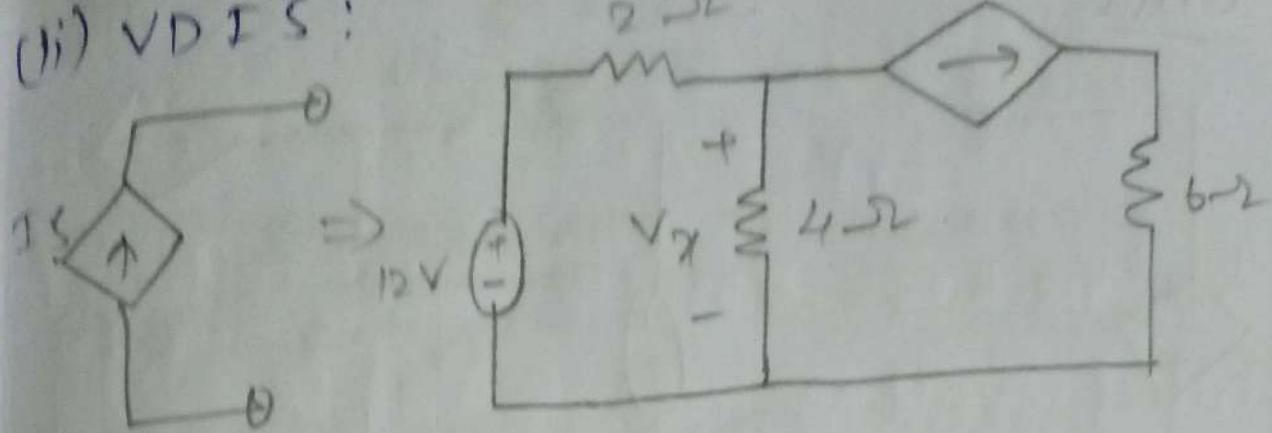

It is a dependent current source which depends on other element voltage in the same circuit.


(iii) CDCS:

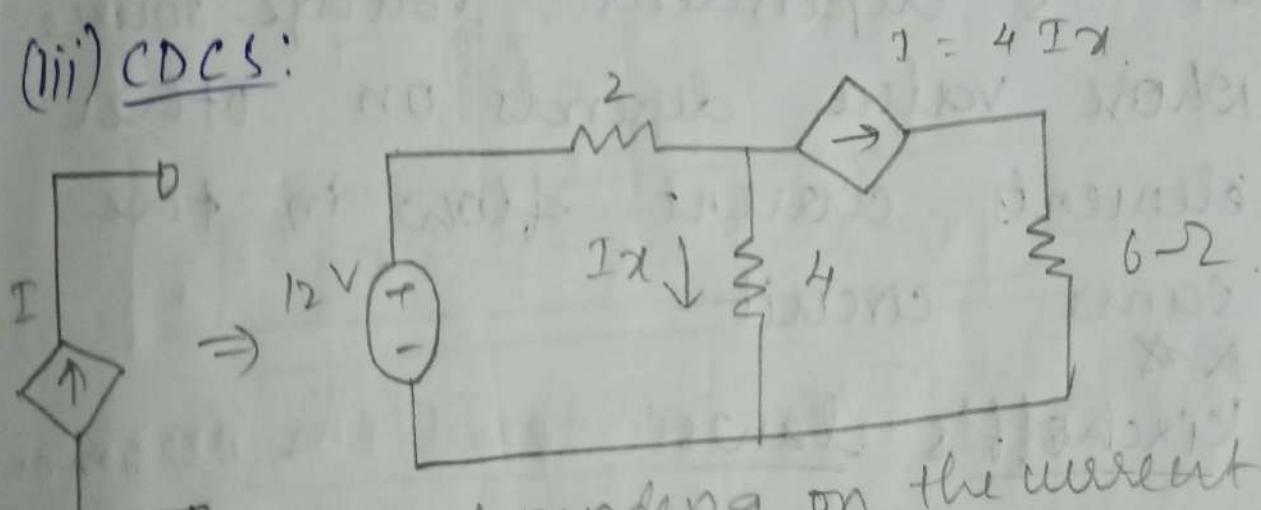

depending on the current from some element in the same circuit.

current dependent current source  
It is dependent current source whose value depends on other elements in the same circuit.

#### 4) CDVS:

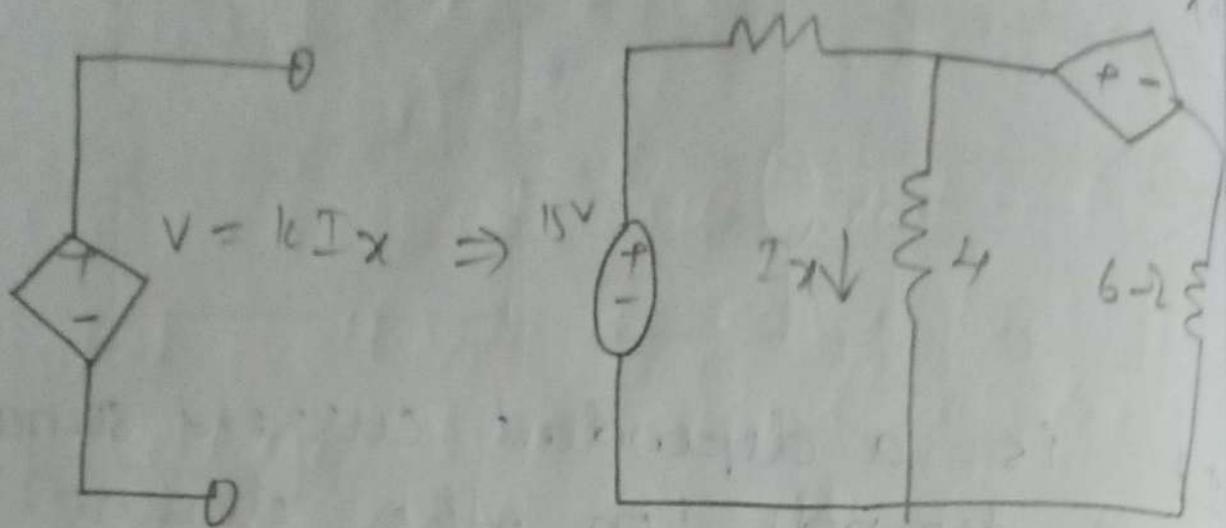

current dependent voltage source  
It is dependent voltage source  
whose value depends on other  
elements current flow in the  
same circuit.

\*\* Kirchoff's laws! problem in exam

① KCL


② KVL

1) Kirchoff's current law:

It states that algebraic sum  
of all the currents meeting at  
a common point or junction or

node is equal to zero  
(or)

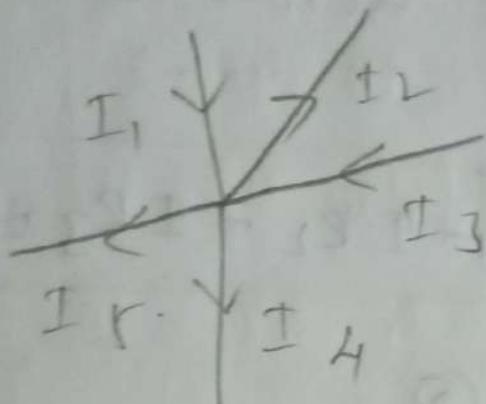
The algebraic sum of incoming currents is equal to algebraic sum of outgoing current.



$$I_1 + I_3 = I_2 + I_4 + I_r \quad \text{--- (1)}$$

$$I_1 + I_3 - I_2 - I_4 - I_r = 0 \quad \text{--- (2)}$$

(ii) Kirchoff's Voltage law:

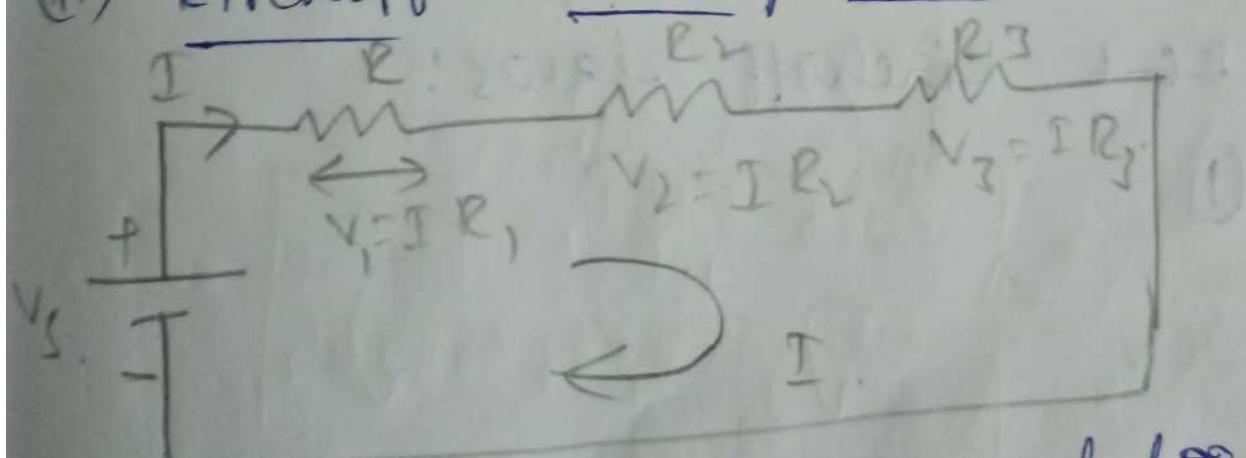

It states that in a closed loop algebraic sum of voltage drop

across the each and every element is equal to zero  
(or)

In a closed loop total voltage total voltage is equal to sum of voltage drop across each & every element.


$$-V_s + IR_1 + IR_2 + IR_3 = 0.$$

→ ①

②

$$V_s = IR_1 + IR_2 + IR_3$$

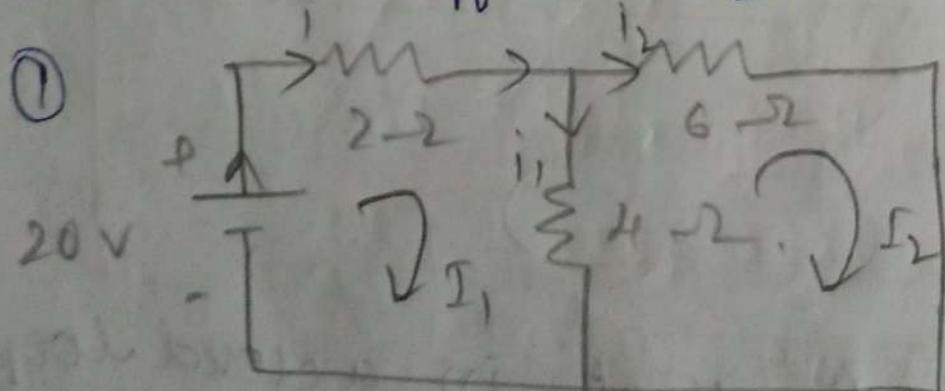Q) Determine current through each and every element using ~~KCL~~ Kirchoff laws!



$$-20V + 2i_1 + i_1 4 + i_2 6.$$

Applying KVL to loop 1

$$-20 + 2I_1 + 4(I_1 - I_2) = 0$$

$$2I_1 + 4I_1 - 4I_2 = 20.$$

$$6I_1 - 4I_2 = 20 \quad \text{---(1)}$$

Applying KVL to loop 2.

$$6I_2 + 4(I_2 - I_1) = 0.$$

$$6I_2 + 4I_2 - 4I_1 = 0.$$

$$-4I_1 + 10I_2 = 0.$$

$$2(3I_1 - 2I_2 = 10)$$

$$3(-2I_1 + 5I_2 = 0)$$

$$6I_1 - 4I_2 = 20.$$

$$-6I_1 + 15I_2 = 0$$

---

$$11I_2 = 20.$$


$$I_2 = \frac{20}{11}.$$

$$-2I_1 + 10\left(\frac{20}{11}\right) = 0.$$

$$-24I_1 + 200 = 0$$

$$I_1 = \frac{50}{11} - 10V + 4(I_2 - I_1)$$

1) Determine  $I$  value from the circuit.

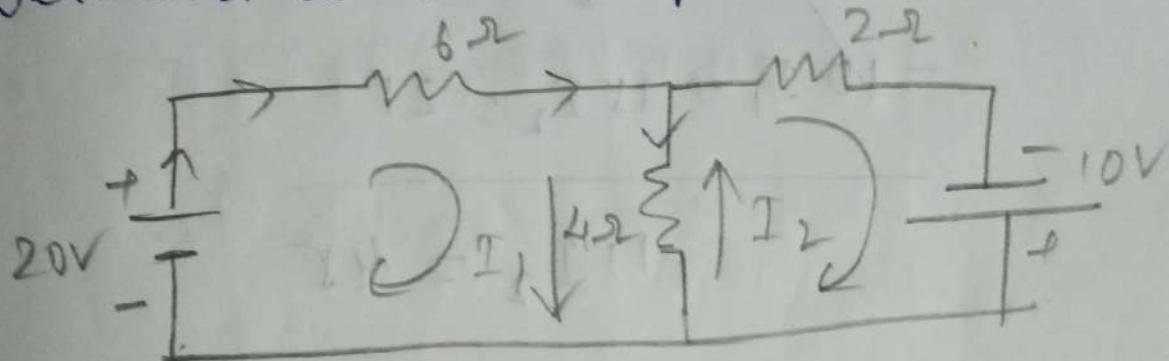

loop 1

$$-20 + 6I_1 + 4(I_1 - I_2) = 0.$$

$$6I_1 + 4I_1 - 4I_2 = 20.$$

$$10I_1 - 4I_2 = 20.$$

$$3(5I_1 - 2I_1 = 10)$$

loop 2

$$2I_2 - 10 + 4(I_2 - I_1) = 0.$$

$$2I_2 - 4I_1 - 10 = 0.$$

$$5(3I_2 - 2I_1 = 5)$$

$$2(5I_1 - 2I_2 = 10)$$

$$5(-2I_1 + 3I_2 = 5)$$

$$10I_1 - 4I_2 = 20$$

$$-10I_1 + 15I_2 = 25$$

$$\underline{11I_2 = 45}$$

$$I_2 = \frac{45}{11}$$


$$5I_1 - 2\left(\frac{45}{11}\right) = 10.$$

$$55I_1 - 90 = 110.$$

$$55I_1 = 200$$

$$I_1 = \frac{200}{55} 40.$$

$$I_1 = \frac{40}{11}$$

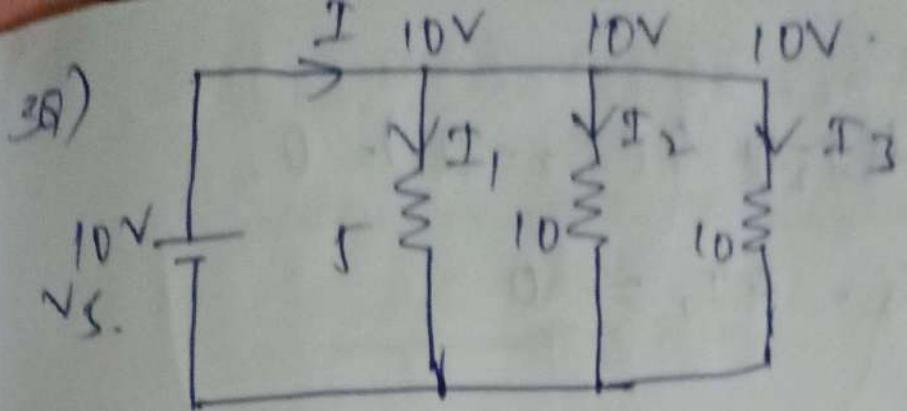

find out the value of  $I$


$\rightarrow$  KCL

$$\rightarrow I = I_1 + I_2 + I_3.$$

$$= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}.$$

$$I = \frac{10}{5} + \frac{10}{10} + \frac{10}{10}.$$

$$= 2 + 1 + 1 \\ \boxed{I = 4A}$$

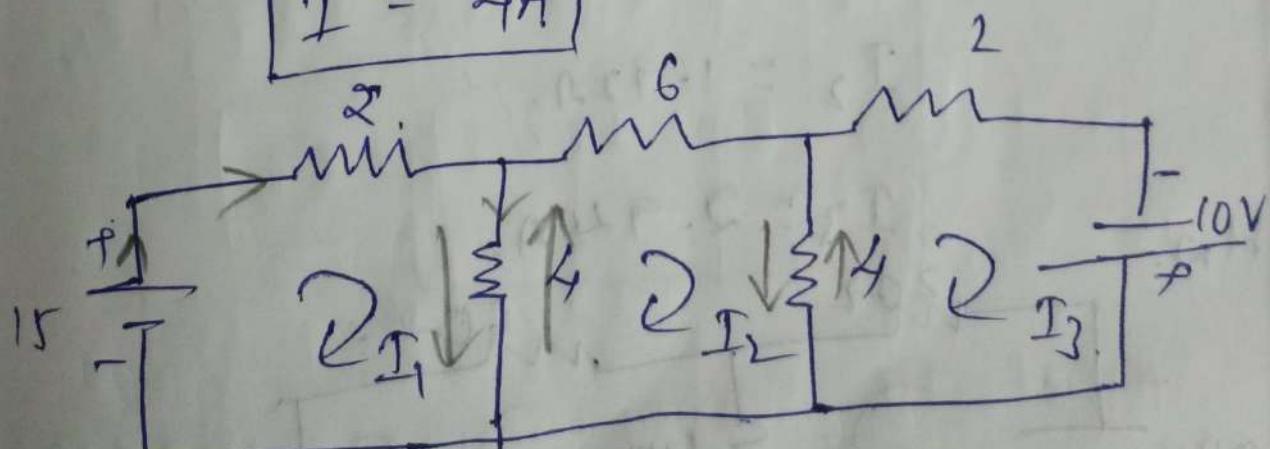

$$-15 + 2I_1 + 4(I_1 - I_2) = 0.$$

$$6I_1 - 4I_2 = 15$$

loop 2:

$$6I_2 + 4(I_2) + 4(I_2 - I_1) = 0.$$

$$6I_2 + 8I_2 - 4I_1 = 0$$

$$14I_2 - 4I_1 = 0.$$

loop 3:

$$14I_2 - 4I_1 + 4I_3 = 0. \quad \textcircled{1}$$

$$2I_3 - 20 + 4(I_3 - I_2) = 0.$$

$$2I_3 - 10 + 4I_3 - 4I_2 = 0.$$

$$6I_3 - 4I_2 = 10.$$


$$3I_3 - 2I_2 = 5. \quad \textcircled{2}$$

$$I_1 = 3.78A.$$



$$I_2 = 1.92A.$$

$$I_3 = 2.94A.$$

H.W.

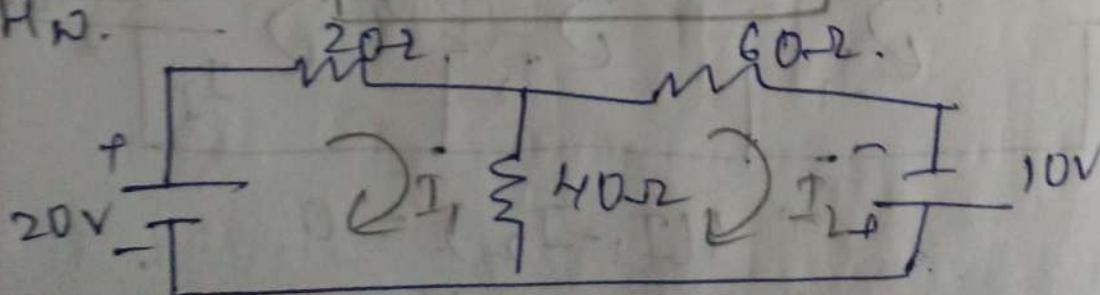

→ Resistors - Series Connection!

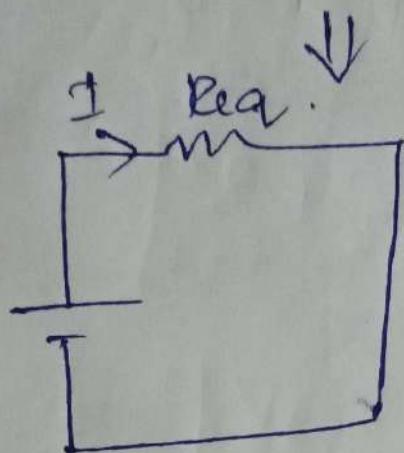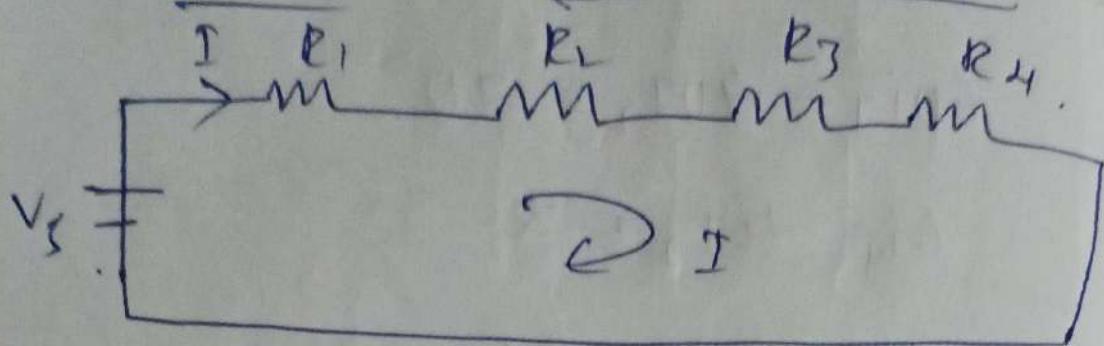

Equivalent circuit

$$-V_s + V_1 + V_2 + V_3 + V_4 = 0.$$

$$V_1 + V_2 + V_3 + V_4 = V_s.$$

$$I \cdot Req = I \cdot R_1 + I \cdot R_2 + I \cdot R_3 + I \cdot R_4.$$


$$\boxed{Req = R_1 + R_2 + R_3 + R_4.}$$

In series connection  $Req$  is equal to summation of all resistors.

Q) Consider a series, resistive circuit in which two resistors  $r_1, r_2$

are connected in series across one voltage source in these series circuits current is constant voltage drop across each resistor is given by  $IR$ .

Voltage division principle:

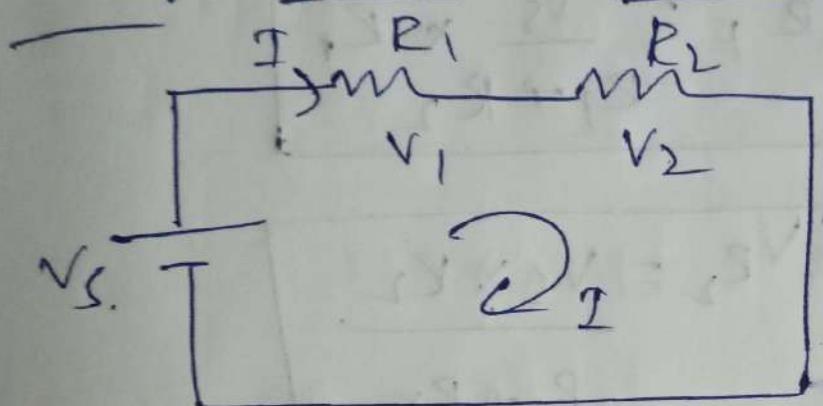

Consider a series resistive circuit in which  $R_1$  &  $R_2$  are connected in series across a single voltage source. Here, since the circuit is series current is constant

$$-V_s + V_1 - V_2 = 0$$

$$V_s = V_1 + V_2$$

$$V_s = IR_1 + IR_L$$

$$V_S = I(R_1 + R_2)$$


$$I = \frac{V_S}{R_1 + R_2}$$

$$V_1 = IR_1$$

$$\boxed{V_{R_1} = \frac{V_S}{R_1 + R_2} \times R_1}$$

$$\boxed{V_{R_2} = \frac{V_S \times R_2}{R_1 + R_2}}$$

resistor - parallel combination:

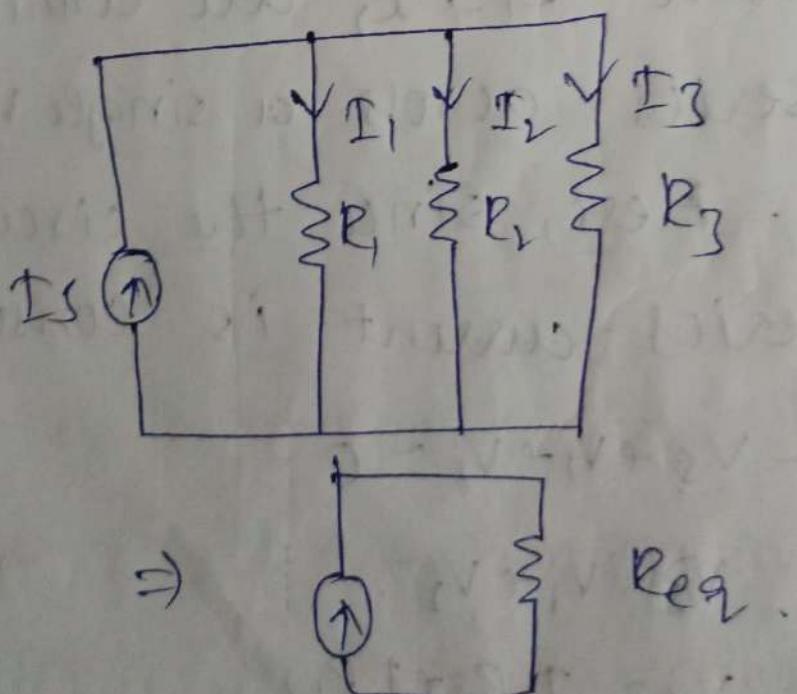

$$KCL = I_1 + I_2 + I_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I_S = \frac{V}{R_{eq}}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

If  $n$  resistors are connected in parallel.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

current division principle!

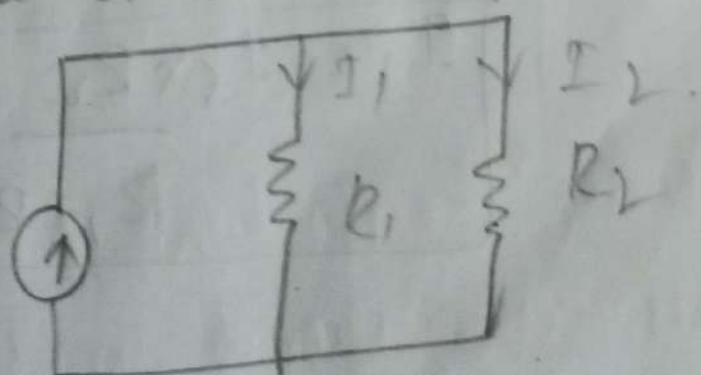current across single element in the circuit



ccL

$$I_S = I_1 + I_2$$

$$V_S = V_1 = V_2$$

$$V_1 = V_2$$

$$I_1 R_1 = I_2 R_2$$

$$I_1 = \frac{I_2 R_2}{R_1}$$

$$I_S = I_1 + I_2$$

$$= \frac{I_2 R_2}{R_1} + I_2$$


$$I_S = I_2 \left( \frac{R_2 + R_1}{R_1} \right)$$

$$\boxed{I_2 = I_S \frac{R_1}{R_1 + R_L}}$$

$$\boxed{I_1 = I_S \frac{R_2}{R_1 + R_L}}$$

problem !

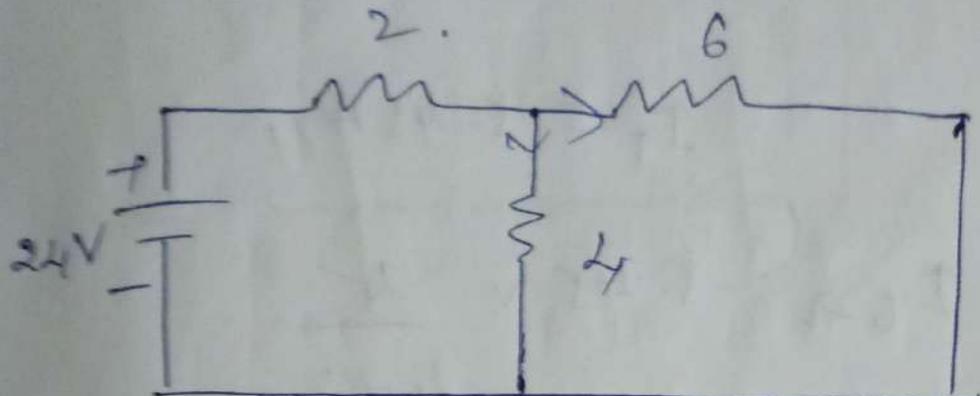- 1) Determine power dissipated by 6 Ohms resistor & using required technique.



$$P = VI.$$

$$\text{Ans} \quad P_{6\Omega} = I_6^2 R.$$

$$I_6 = I_f \times \frac{4}{4+6}.$$

$$I_f = \frac{V}{R_{eq}}$$

$$R_f \text{ (or) } R_{eq} = \frac{6 \times 4}{6+4} + 2$$

$$= \frac{24}{10} + 2$$

$$R_{eq} = 4.4 \Omega$$

$$I_T = \frac{V}{R_{eq}}$$

$$= \frac{24}{4+4}$$

$$I_T = 5.45 A_{//}$$

$$I_{6\rightarrow 2} = 5.45 \times \frac{4}{4+6}$$

$$= \frac{5.45 \times 4}{10}$$

$$\boxed{I_{6\rightarrow 2} = 2.18 A_{//}}$$


$$P_{6\rightarrow 2} = I_{6\rightarrow 2}^2 R_6$$

$$= (2.18)^2 \times 6$$

$$\boxed{P_{6\rightarrow 2} = 28.51 W_{//}}$$

Q) Determine  $R_{eq}$  b/w A & B terminals as shown in the below

circuit come in final exams

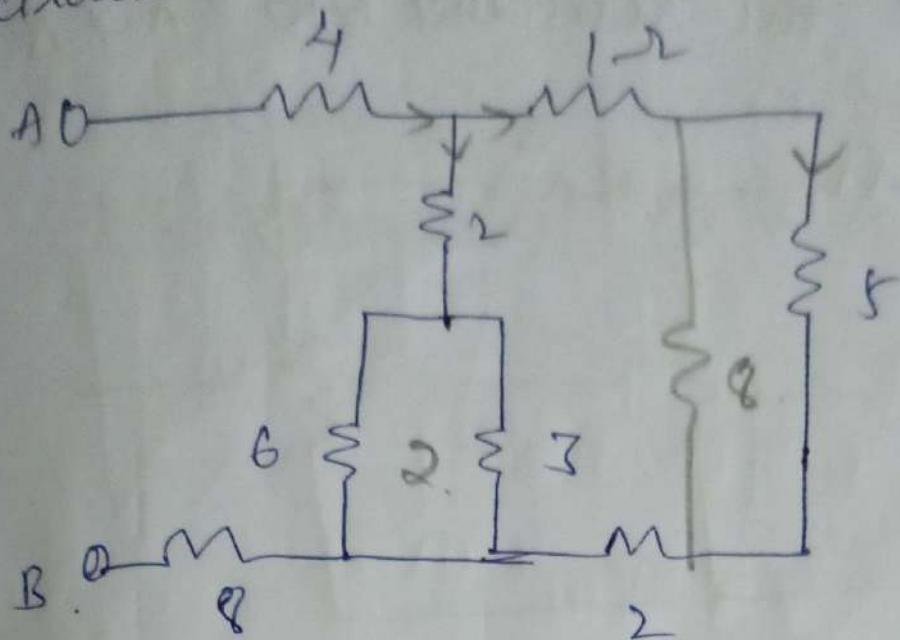



$$1+5+2$$

$$= 8$$

$$2$$


$$\frac{8 \times 3}{9+2}$$

4+

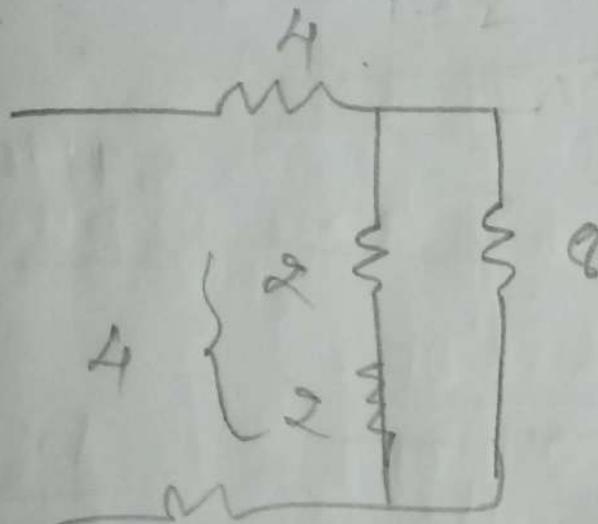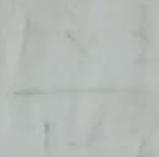

$$\frac{32}{4+8}$$


$$\frac{32}{12} 8$$

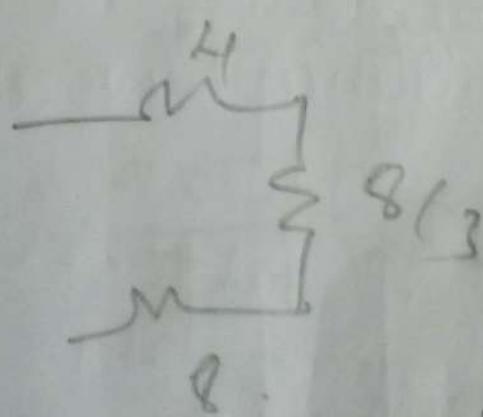

$$4+8/3+8$$


$$R_{AB} = 14.6 - 2$$

B) Evaluate the resistance between A & B

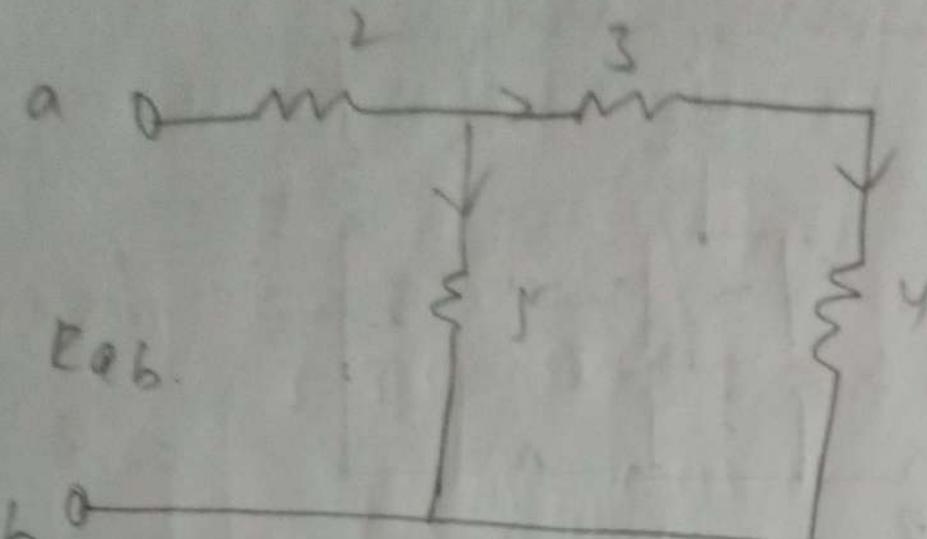

3, 4 series

$$3+4=7$$

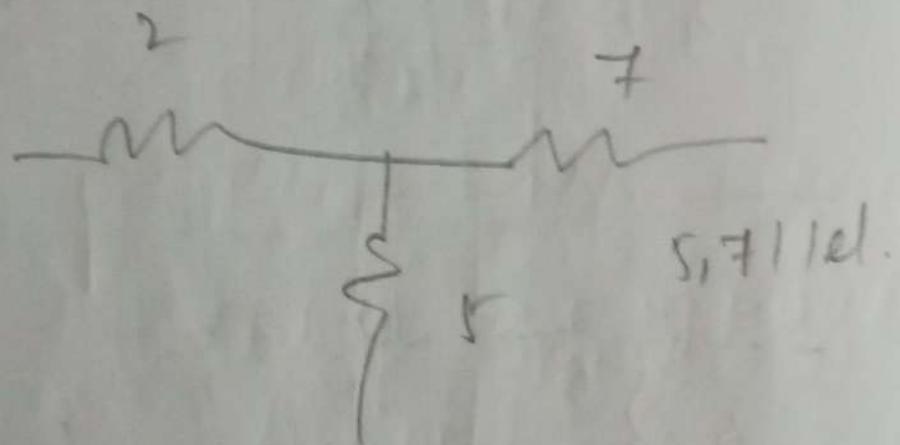

$$35$$

$$\frac{5 \times 7}{5+7}$$

$$2 + \frac{35}{12}$$

$$\frac{35}{12}$$


$$\frac{24 + 35}{12} = \frac{59}{12}$$

$$R_{ab} = 4.91$$

\* Always sort out series from net

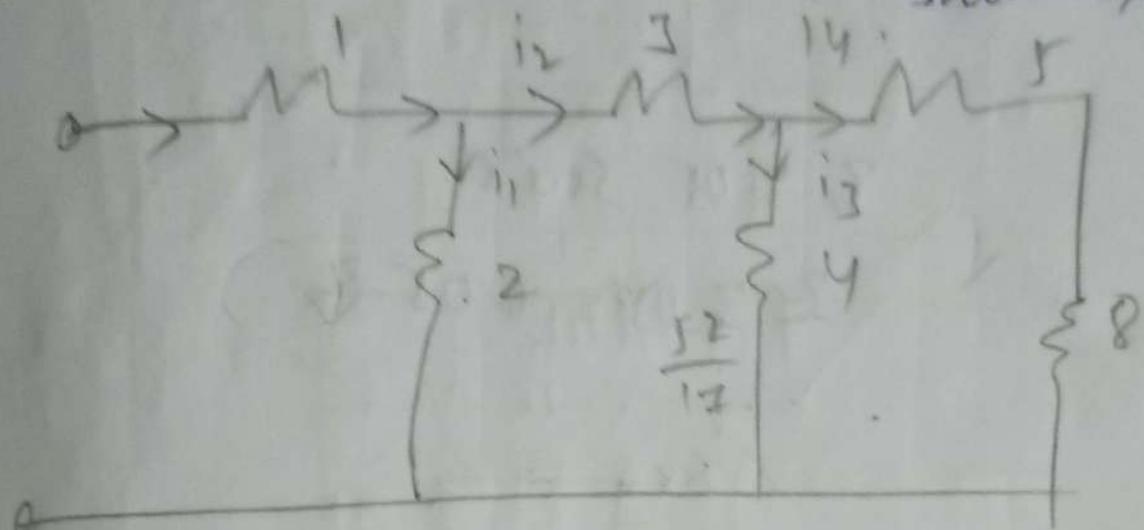
g) calculate the resistance b/w

A B terminals of the circuit below shown by  $\frac{52}{12}$ .




5, 8 series

$$5 + 8 = 13$$

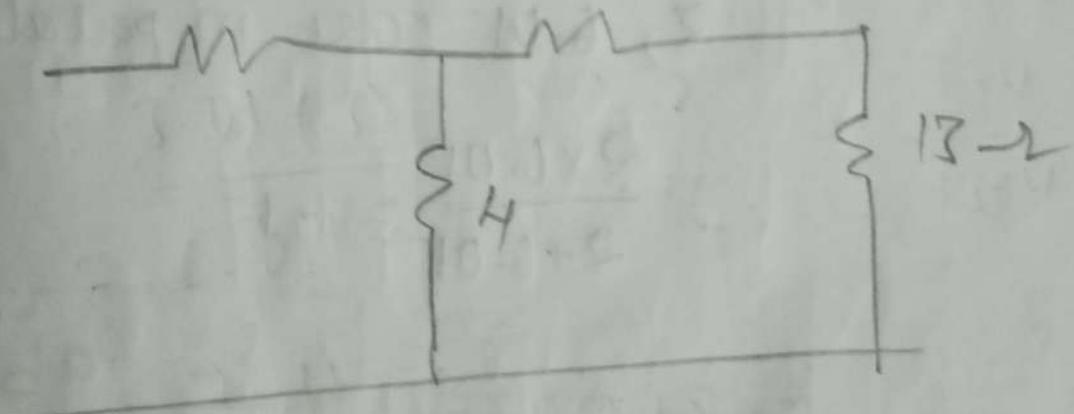


4, 13 parallel
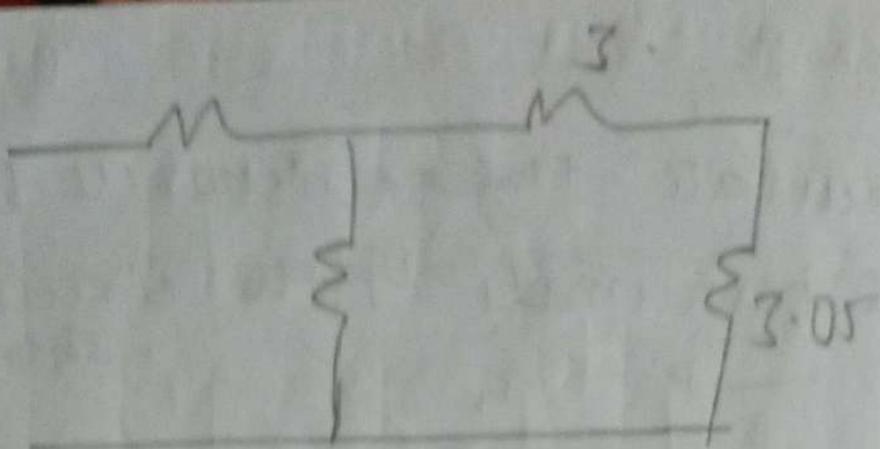
$$\frac{4 \times 13}{4 + 13} = 3.05 \Omega$$



3, 3.05 series.

$$3 + 3.05 = 6.05 \Omega$$

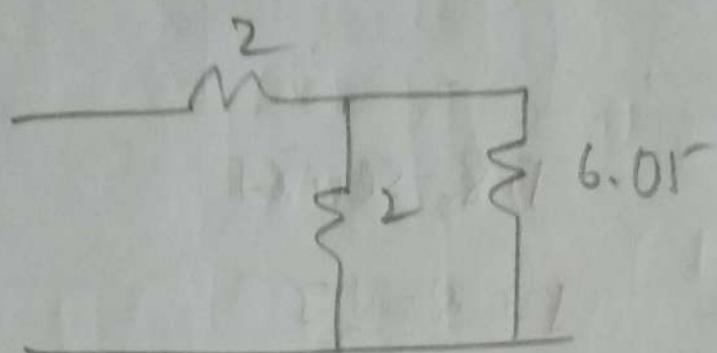


2, 6.05 are in parallel



$$\frac{2 \times 6.05}{2 + 6.05} = 1.5 \Omega$$

$$1.5 = 2.5 = R_{ab}$$

6 marks.

Q) Evaluate resistance b/w ab terminals.

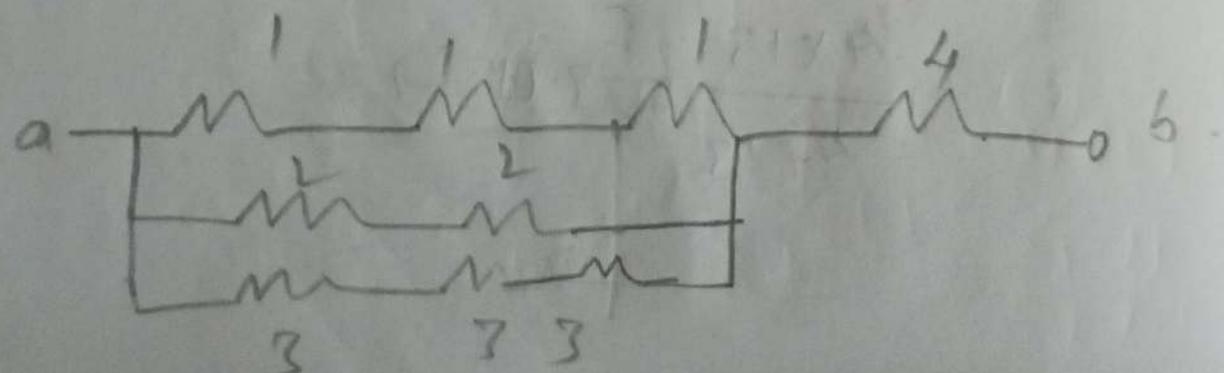

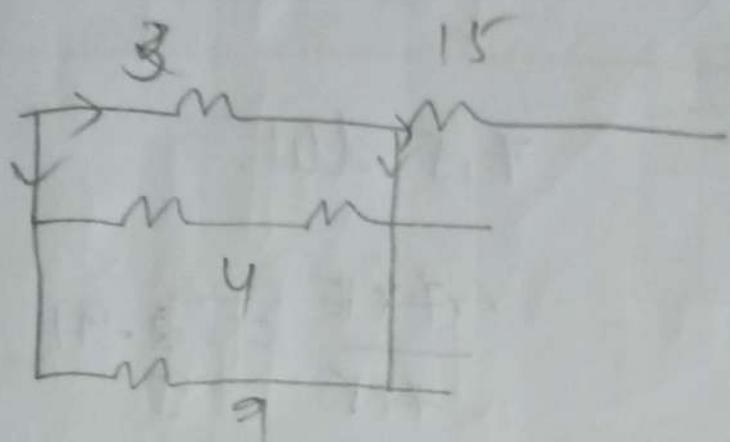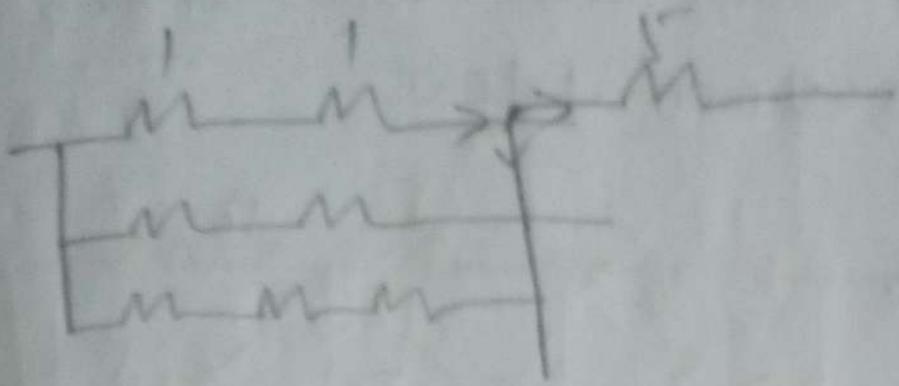

$$\frac{12}{7} \times 9 - 115 \quad \frac{3 \times 4}{7} = \frac{12}{7}$$


$$\frac{1.7 \times 9}{1.7 + 9} - 115$$

$$\frac{15.3}{10.7} - 115$$

$$1.42 - 4.$$


$$R_{ab} = 5.42\Omega$$

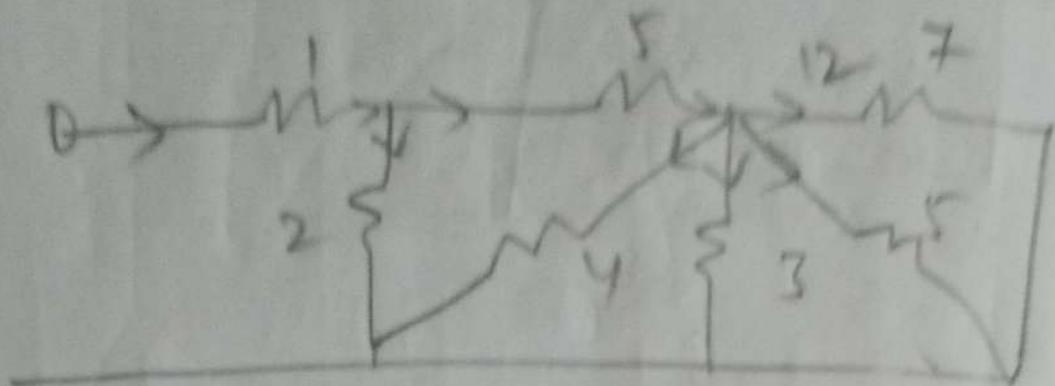Calculate the total resistance of the circuit shown below:




$$7.5 \text{ m}.$$


$$\frac{7 \times 15}{7+15} = 2.91$$

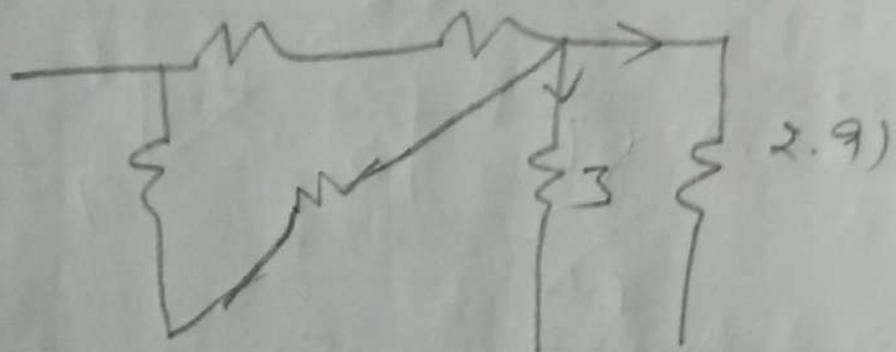

$$\frac{3 \times 2.91}{3+2.91} = 1.5$$

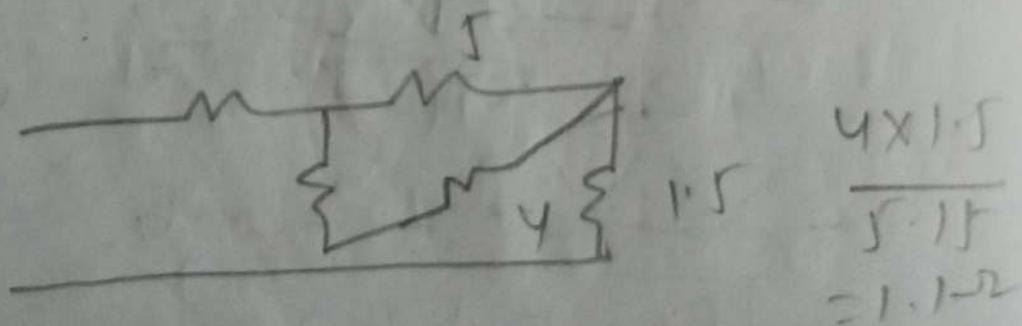


$$\frac{4 \times 1.5}{5.15} = 1.12$$

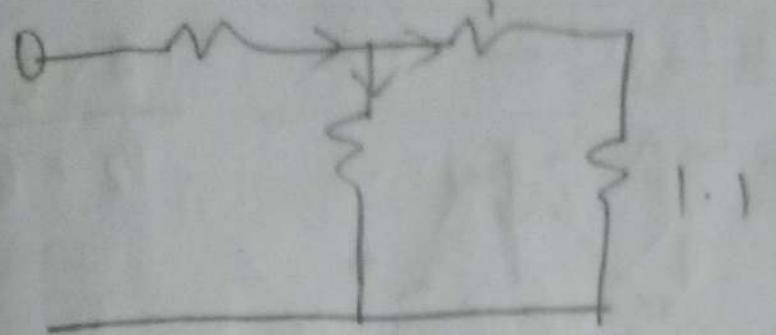


$$6.1 = 6.1$$

1.1

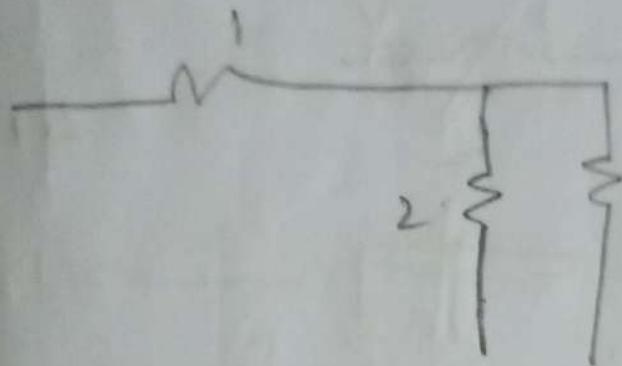

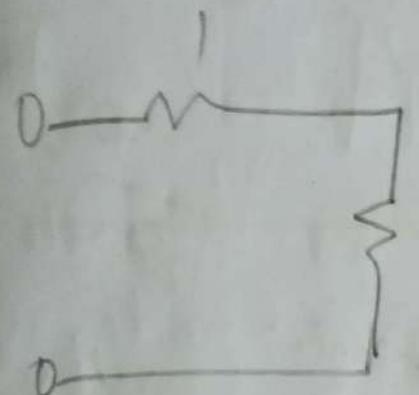
$$6.1 = \frac{2 \times 6.1}{2 + 6.1} = 1.5$$




1.1

$$1 + 1.5 = 2.5$$


$$\boxed{2.5 = R_{ab}}$$

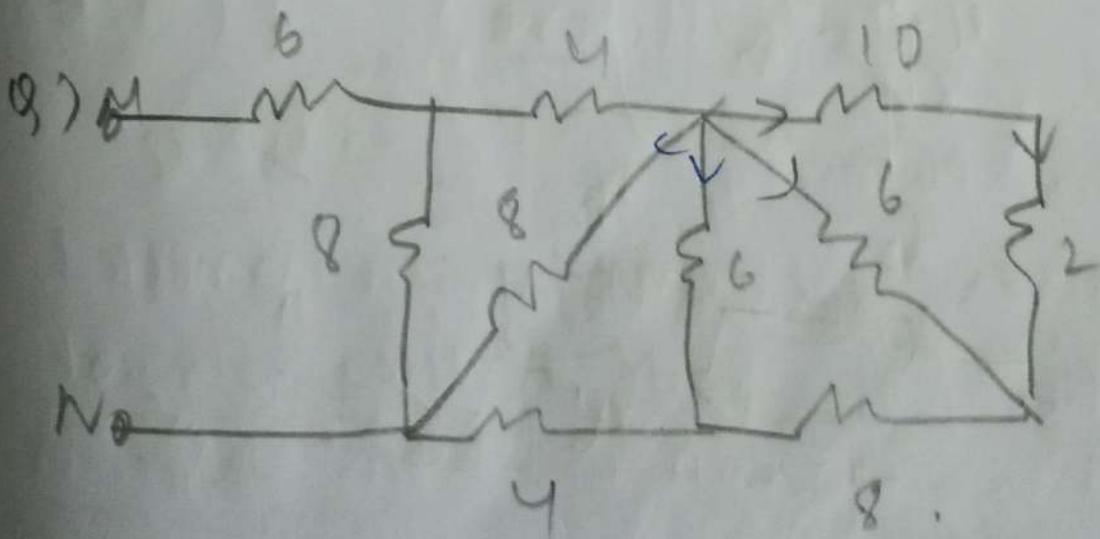

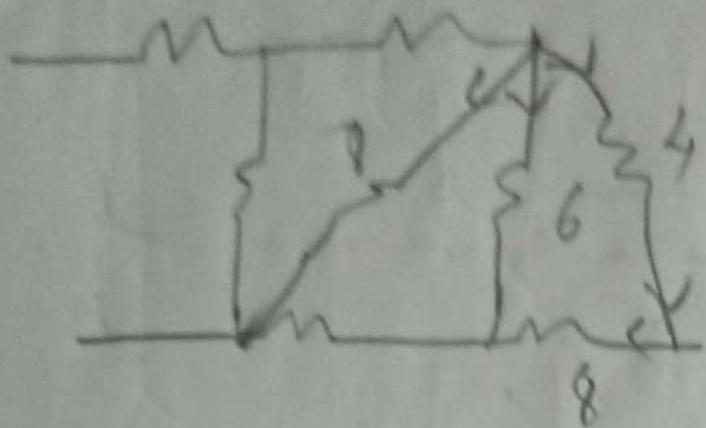


$$\frac{12+6}{12+6}$$


$$4+8$$

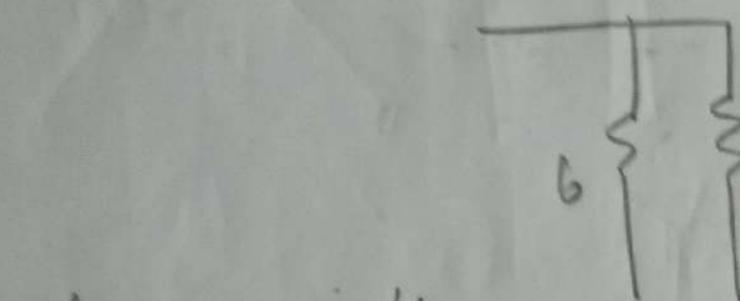

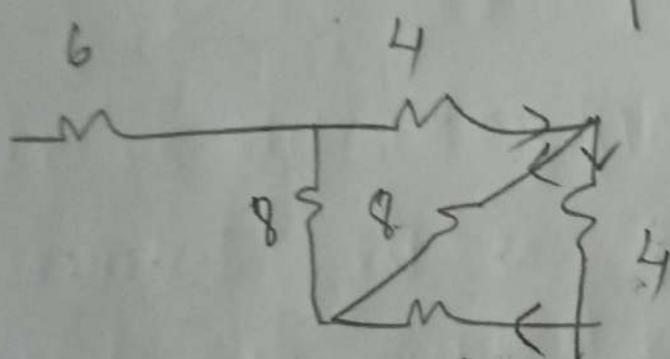
$$\frac{12 \times 4}{12+4} = \frac{48}{16}$$



$$\frac{4+8}{4+8}$$

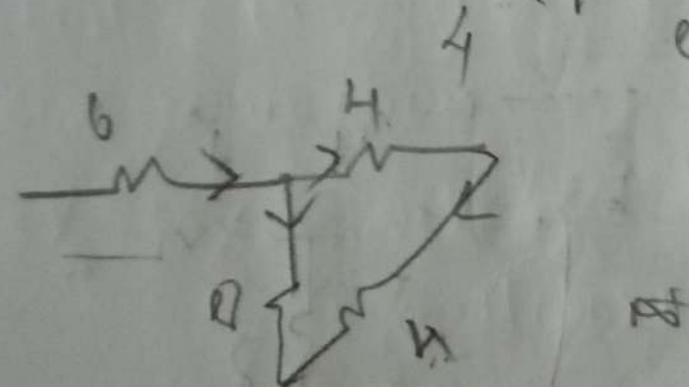


$$\frac{32}{12}$$

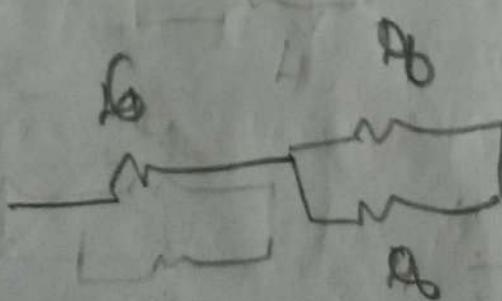


$$\frac{4}{4}$$

$$\frac{16}{16} = 10$$

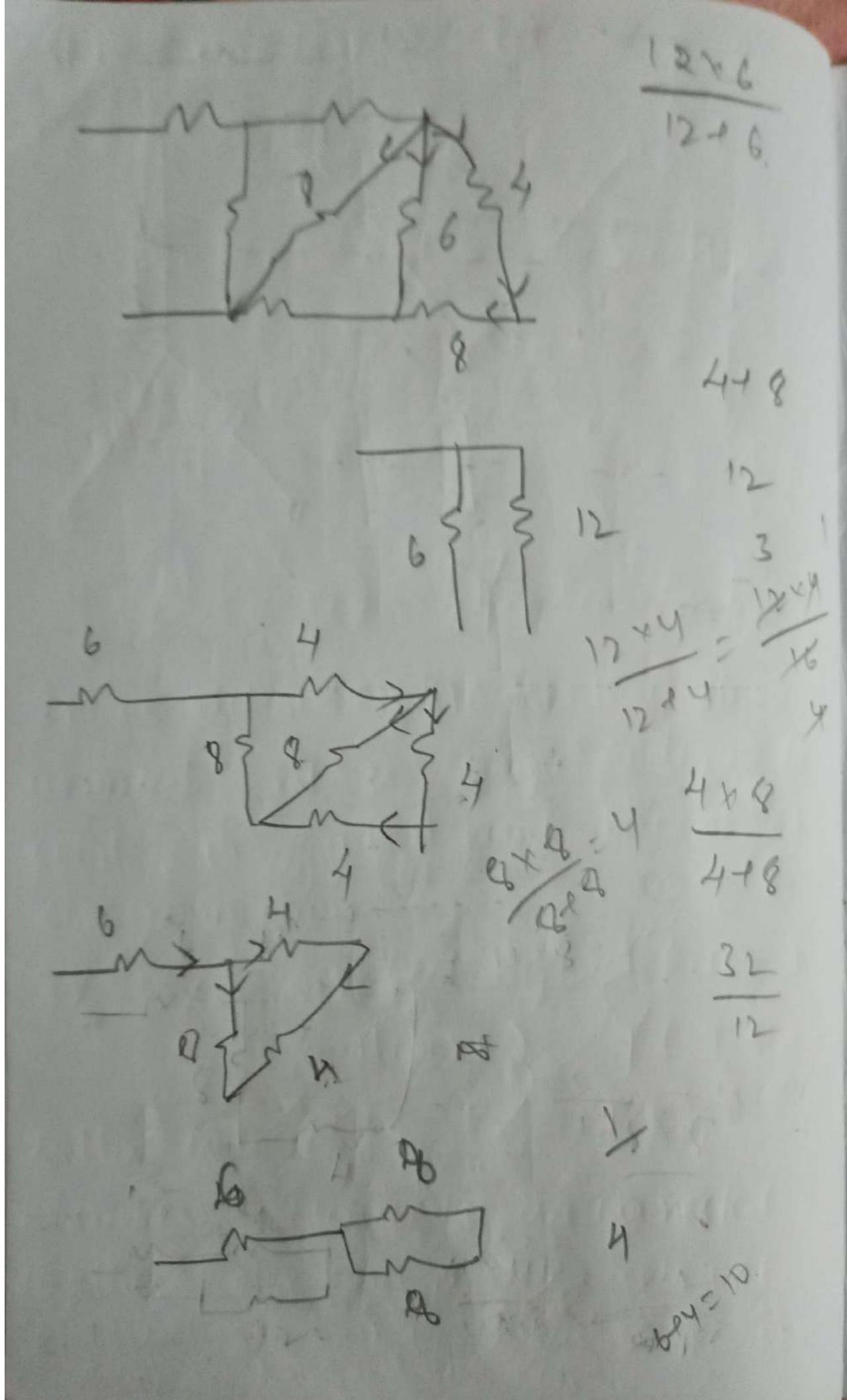

## Star Connection!

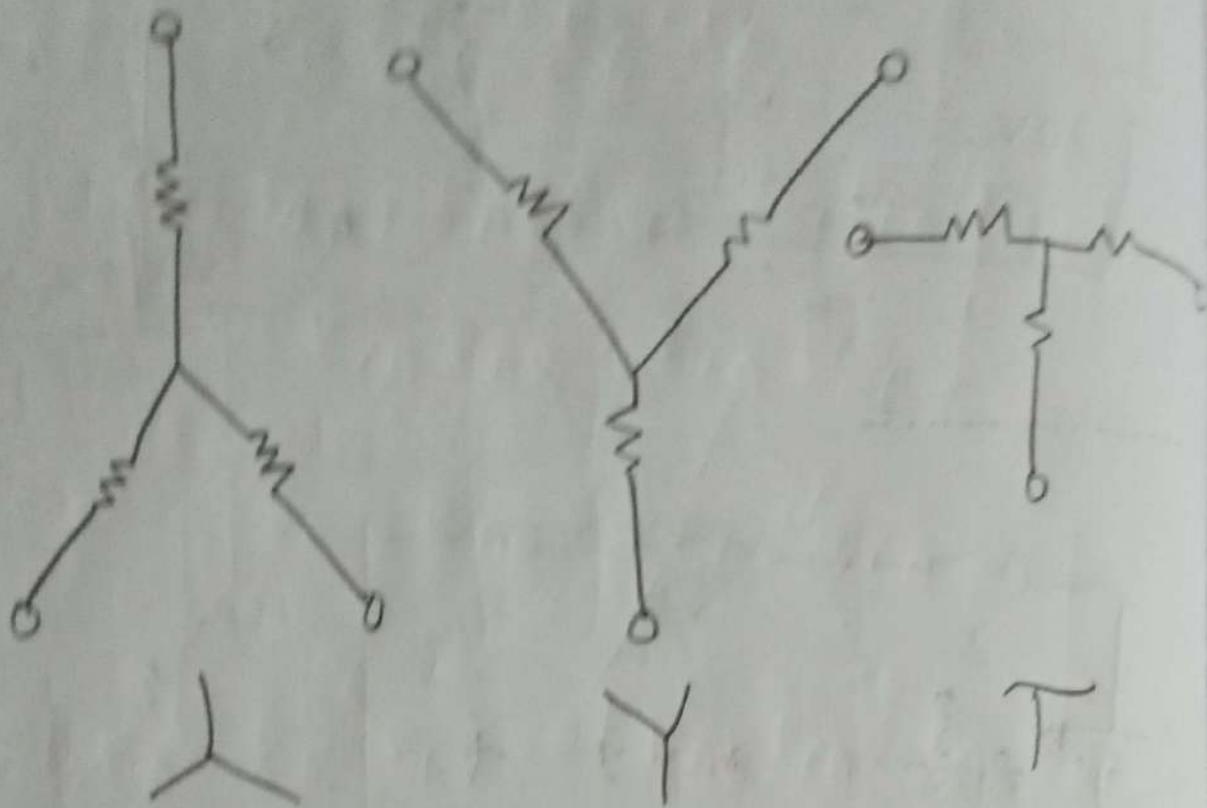



It is defined as the three elements connected at a single node, node point or neutral point known as star connection.

It is represented by  $\begin{array}{c} \text{I} \\ \backslash / \end{array}$  (star)  
 $\begin{array}{c} \text{Y} \\ \backslash / \end{array}$  (Y-network)  $\begin{array}{c} \text{T} \\ \diagup \diagdown \end{array}$  (T-Shape)

## Delta Connection:


Whenever 3 elements are connected together it forms a delta network either it will be  $\Delta$  shape or  $\nabla$  shape.

Delta Connection: 3 elements are taken

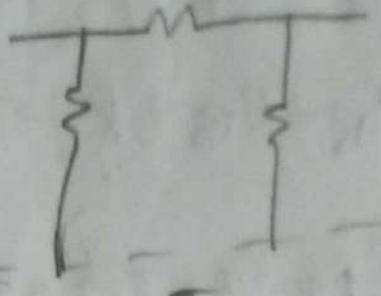
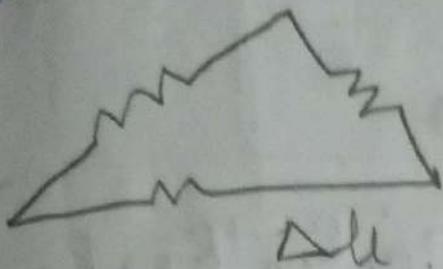


and connected together as a closed loop.

Delta to Star Connection:

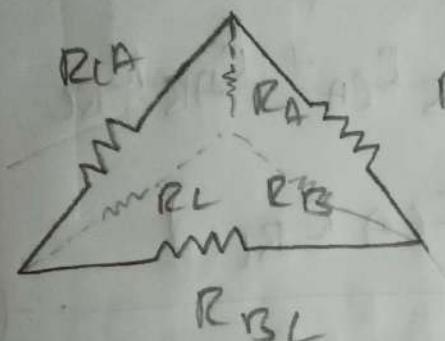

$$R_{AB} \Rightarrow$$

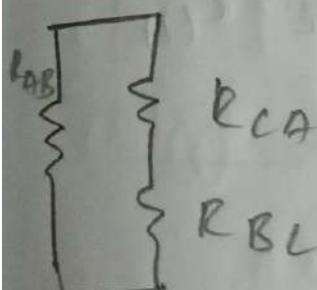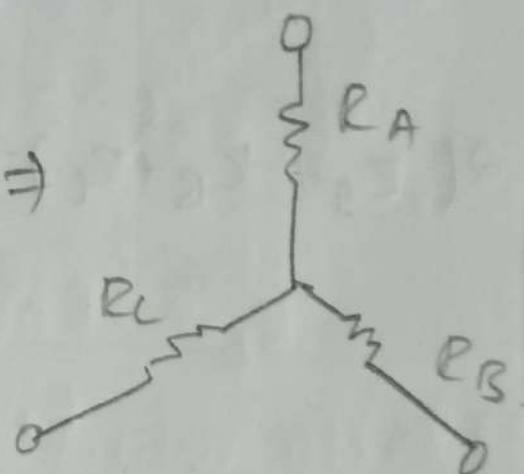

$$R_{AB} + R_B$$

$$= \frac{R_{AB} \parallel (R_A + R_{BC})}{R_{AB} + R_{BC} + R_A}$$

$$R_{AB} + R_{BC} + R_A$$

$$R_B + R_C = \frac{R_{BC} \parallel (R_A + R_{AB})}{R_{AB} + R_{BC} + R_A} \quad \text{--- (2)}$$

$$R_{AB} + R_{BC} + R_A$$

$$R_C + R_A = \frac{R_A \parallel (R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_A} \quad \text{--- (3)}$$

$$R_{AB} + R_{BC} + R_A$$

Adding ① + ② + ③

$$R_A + R_B + R_C + R_C + R_A$$

$$\begin{aligned} &= R_{AB} R_{CA} + R_{AB} R_{BC} + R_{BC} R_{CA} + R_{RC} R_{AB} \\ &\quad + R_{CA} R_{AB} + R_{CA} R_{BC} \end{aligned}$$

$$R_{AB} + R_{BC} + R_{CA}$$

$$2(R_A + R_B + R_C) = 2(R_{AB} R_{CA} + R_{AB} R_{BC}$$

$$+ R_{CA} R_{BC})$$

$$R_{AB} + R_{BC} + R_{CA}$$

$$④ - ①$$

$$R_A + R_B + R_C - R_A - R_B$$

$$\begin{aligned} &= R_{AB} R_{CA} + R_{AB} R_{BC} + R_{CA} R_{BC} \\ &\quad - R_{AB} R_{CA} - R_{AB} R_B \end{aligned}$$

$$R_{AB} + R_{BC} + R_{CA}$$

$$\begin{aligned} &- \frac{R_{AB} R_{CA} + R_{AB} R_B}{R_{AB} + R_{BC} + R_{CA}} \end{aligned}$$

$$R_C = \frac{R_{CA} R_{BL}}{R_{AB} + R_{BL} + R_{CA}}$$

$$\textcircled{4} - \textcircled{1}$$

$$R_A + R_B + R_C - R_B - R_C$$

$$= R_{AB} R_{CA} + R_{AB} R_{BL} + R_{CA} R_{BL} \\ - R_{BL} R_{CA} - R_{BL} R_{AB} \\ \hline R_{AB} + R_{BL} + R_{CA}$$

$$R_A = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BL} + R_{CA}}$$


$$\textcircled{4} - \textcircled{1}$$

$$R_A + R_B + R_C - R_A - R_C$$

$$= R_{AB} R_{CA} + R_{AB} R_{BL} + R_{CA} R_{BL} \\ - R_{AB} R_{CA} - R_{CA} R_{BL} \\ \hline R_{AB} + R_{BL} + R_{CA}$$

$$R_S = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

Star to  $\Delta$  transformation:

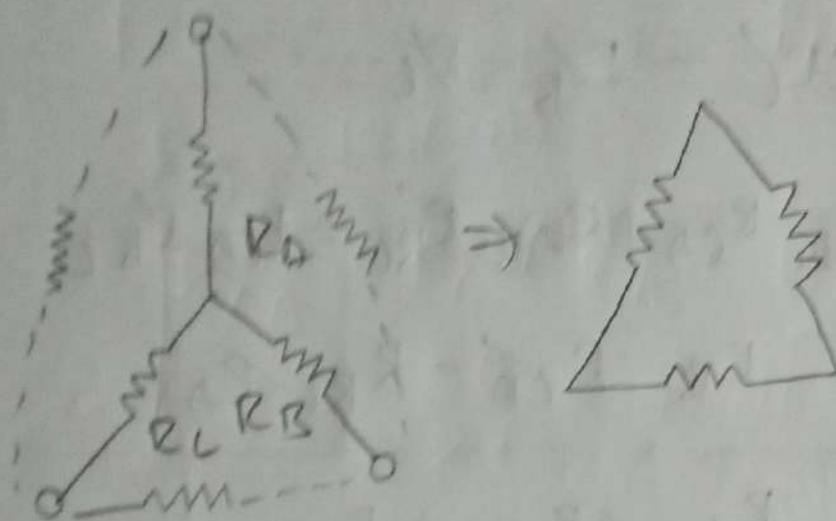

$$R_D = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad - \textcircled{1}$$

$$R_B = \frac{R_{BC} R_{AB}}{R_{AB} + R_{BC} + R_{CA}} \quad - \textcircled{2}$$

$$R_C = \frac{R_{CA} R_{BC}}{R_{AB} + R_{BC} + R_{CA}} \quad - \textcircled{3}$$

$$\textcircled{1} \textcircled{2} + \textcircled{2} \textcircled{3} + \textcircled{3} \textcircled{1}$$

$$R_A R_B + R_B R_C + R_C R_A$$

$$= \frac{R_{AB} R_{CA} \cdot R_{BC} R_{AB}}{(R_{AB} + R_{BC} + R_{CA})^2} + \frac{R_{BC} R_{AB} R_{CA} R_{BC}}{(R_{AB} + R_{BC} + R_{CA})^2} \\ + \frac{R_{CA} R_{BC} R_{AB} R_{CA}}{(R_{AB} + R_{BC} + R_{CA})^2}$$

$$= \frac{R_{AB} R_{CA} R_{BC} + R_{BC} R_{AB} R_{CA} + R_{CA} R_{AB} R_{BC}}{(R_{AB} + R_{BC} + R_{CA})^2}$$

$$R_A R_C + R_A R_B + R_B R_C$$

$$= \frac{R_{AB} R_{BC} R_{CA} (R_{AB} + R_{BC} + R_{CA})}{(R_{AB} + R_{BC} + R_{CA})^2} - \textcircled{1}$$

4/1

$$\frac{R_C R_A + R_A R_B + R_B R_C}{R_A} = \frac{\cancel{R_{BC} R_{AB} R_{CA}}}{\cancel{R_{AB} + R_{BC} + R_{CA}}} \\ \frac{\cancel{R_{AB} R_{CA}}}{\cancel{R_{AB} + R_{BC} + R_{CA}}}$$

$$\boxed{R_C + R_B + \frac{R_B R_C}{R_A} = R_{BC}}$$

$$\boxed{R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}}$$

$$\boxed{R_{CA} = R_C + R_A + \frac{R_C R_A}{R_B}}$$

Problem:

- Q) Delta values are given by  $2\Omega$ ,  $3\Omega$ , and  $4\Omega$  resistances find star values


$$R_{AB} = 2\Omega$$

$$R_{BC} = 3\Omega$$

$$R_{CA} = 4\Omega$$

$$R_A = \frac{(2)(4)}{2+3+4}$$

$$= \frac{8}{9} \Omega = 0.88 \Omega$$

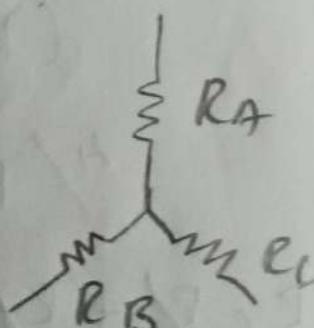

$$R_B = \frac{(2)(3)}{2+3+4}$$

$$= \frac{6}{9} \\ = 0.66 \Omega$$

$$R_C = \frac{(4)(3)}{2+3+4}$$

$$= \frac{12}{9} \\ = 1.33 \Omega$$

Q) Star values are given by 4 $\Omega$ , 5 $\Omega$ , 6 $\Omega$  find delta values.

$$R_A = 4\Omega, R_B = 5\Omega, R_C = 6\Omega.$$


$$R_{AB} = 4 + 5 + \frac{20}{6} \quad R_{CA} = (4) + 6$$

$$= 9 + 3.3 \quad + \frac{24}{5}$$

$$= 12.33 \Omega \quad = 10 + 4.8$$

$$R_{BC} = 5 + 6 + \frac{30}{4} = 18.5 \Omega \quad = 14.8 \Omega$$
$$= 18.5 \Omega$$

Q)

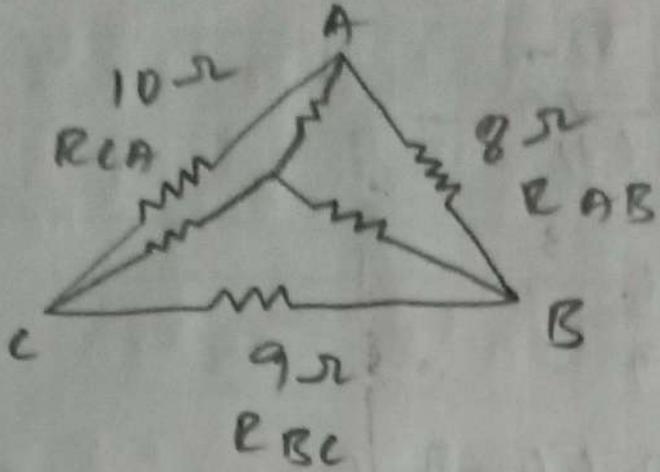

star from  
delta.

$$R_A = \frac{(8)(10)}{8+9+10}$$

$$= \frac{80}{27} = 2.96 \Omega$$

$$R_B = \frac{(8)(9)}{10+9+8}$$



$$= \frac{72}{27}$$

$$= 2.66 \Omega$$

$$R_C = \frac{(10)(9)}{27}$$

$$= \frac{90}{27}$$

$$= 3.33 \Omega$$

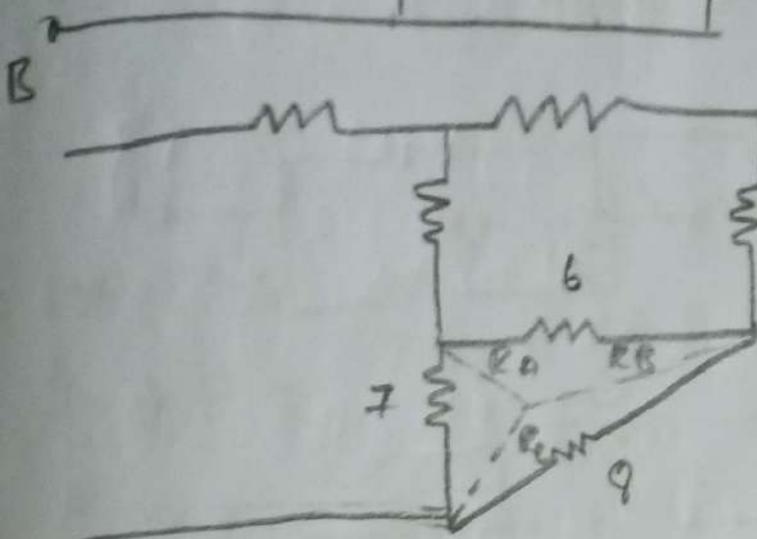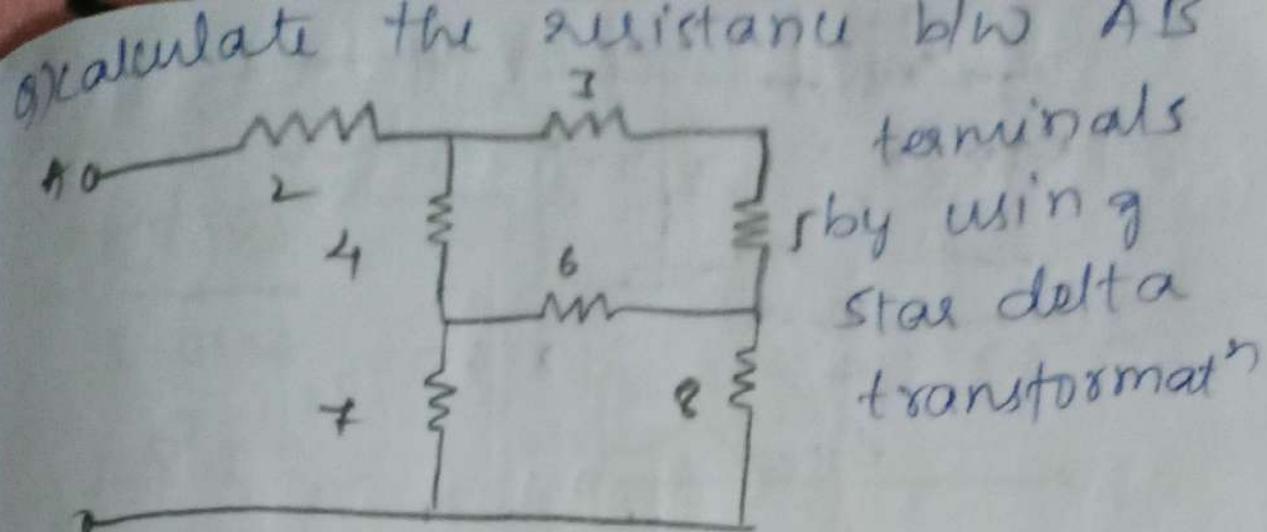

$$R_A = \frac{7 \times 6}{7 + 6 + 8} = 2\Omega$$

$$R_B = \frac{6 \times 8}{7 + 6 + 8} = 2.3\Omega$$

$$R_C = \frac{7 \times 8}{6 + 7 + 8} = 2.6\Omega$$

$$\frac{7+9}{21}$$


$$\frac{1}{10\Omega} + \frac{1}{6}$$

$$\frac{10}{10\Omega} + \frac{1}{6}$$



$$0.0977 +$$

$$0.166.$$


$$= \frac{1}{0.263}$$

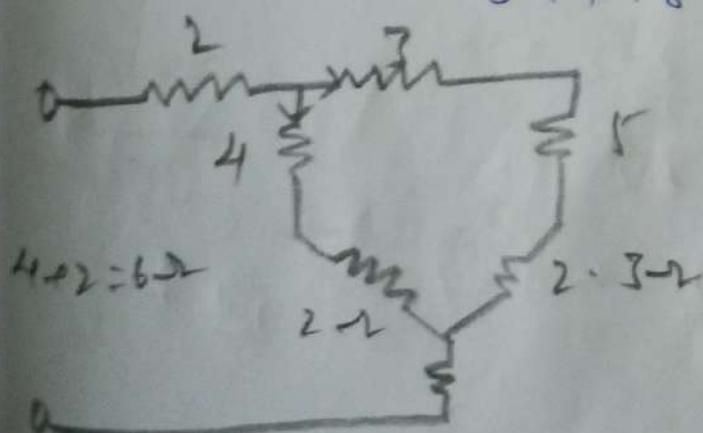

$$3+5+2.3=10.3$$

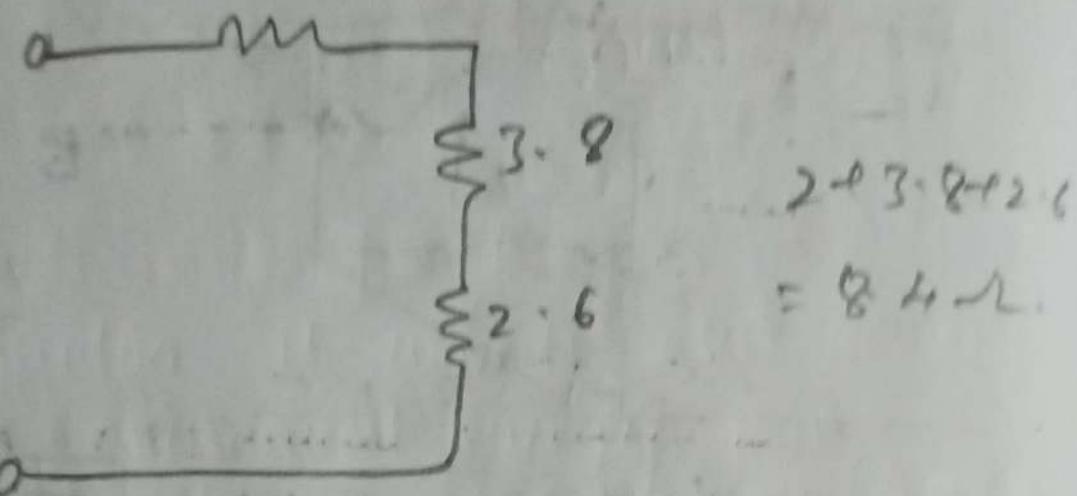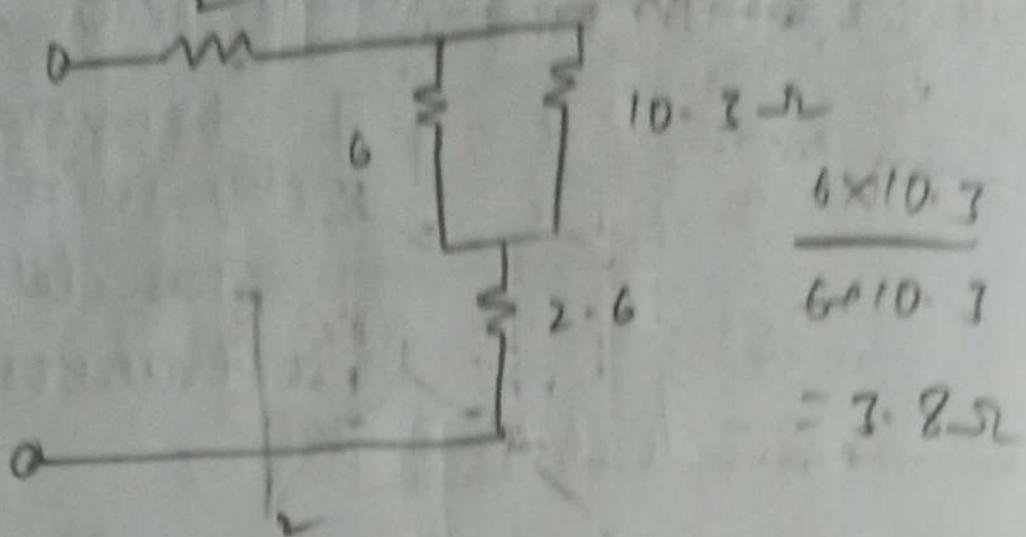


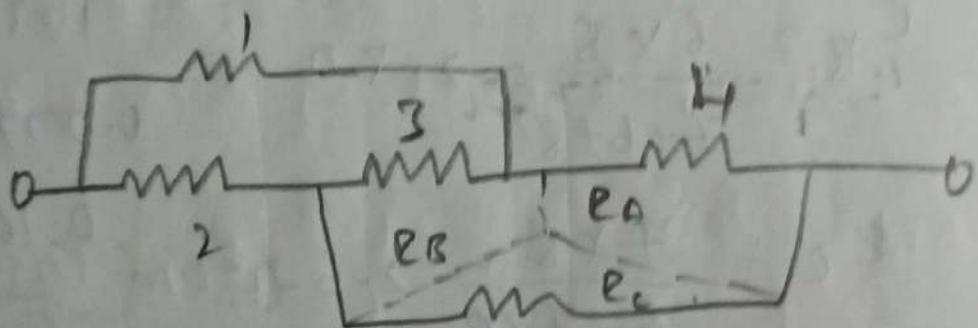Q) calculate resistance b/w AB terminals.




$$\frac{3+5}{12} = \frac{15}{12} = 1.25$$
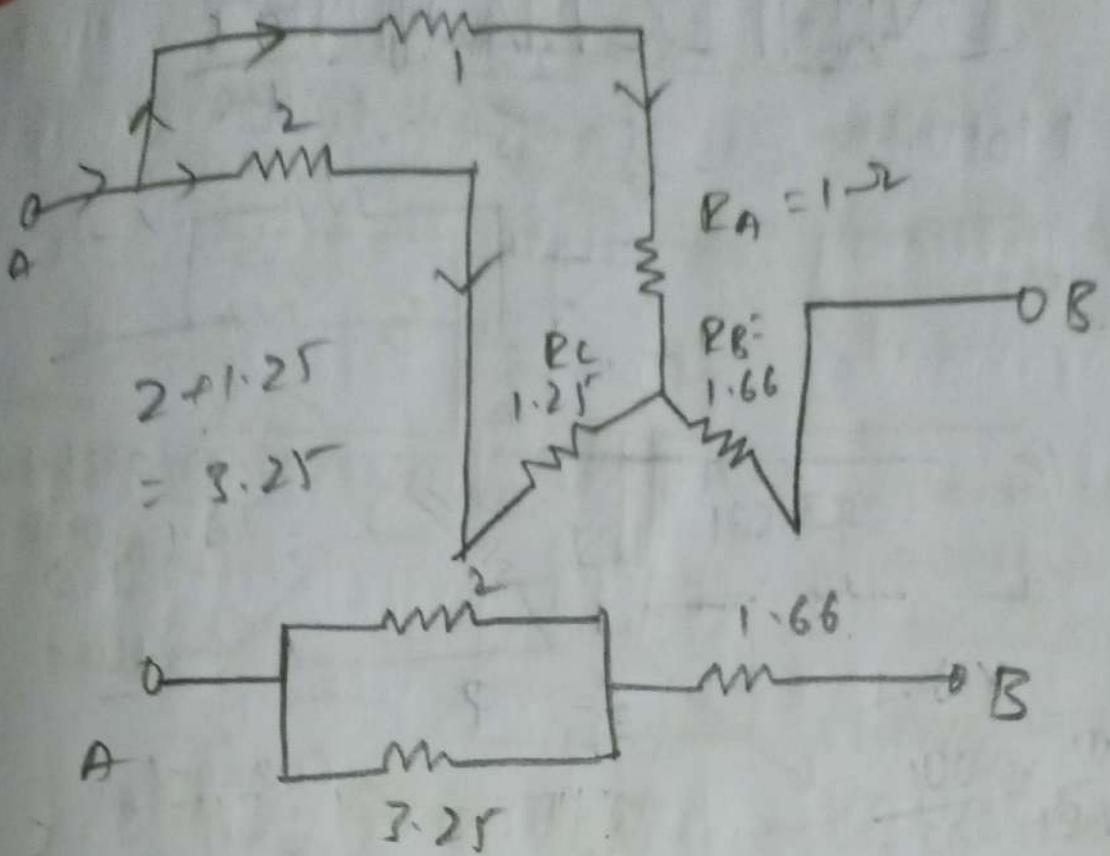
$$R_A = 1 - 2 \cdot \frac{\frac{3+4}{3+4+5}}{\frac{12}{12}}$$


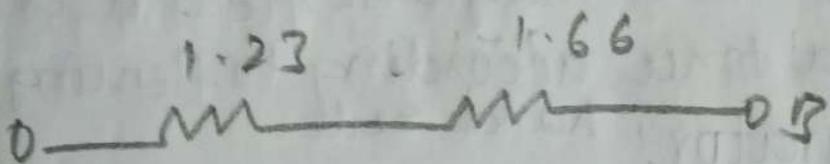
$$\frac{2 \times 3.25}{5.25} = \frac{6.5}{5.25} = 1.23 \Omega$$



$$R_{eq} = 2.89 \Omega$$

DC Machine